

BEE

Basic Electrical Engineering.

Syllabus

Unit - 1

DC - Circuits.

- ⇒ Introduction of Basic electrical elements.
- ⇒ Energy Sources.
- ⇒ KCL and KVL.
- ⇒ Super position theorem.
- ⇒ Thevenin's theorem.
- ⇒ Norton's theorem.

Unit - 2

AC - Circuits.

- ⇒ Single phase AC - circuits consisting of (R, L, C, RL, RC) combination of Series connection.
- ⇒ Single phase AC - circuits consisting of (R, L, C, RL, RC) combination of Parallel connection.

Unit - 3

Transformers.

- ⇒ Construction and Working Principle of transformer.
- ⇒ Losses in transformer.
- ⇒ Regulation and efficiency of transformer.
- ⇒ Construction of three phase transformer.

Unit - 4

Electrical Machines

- Construction and Working principle of Induction motor
- Construction and Working principle of Synchronous generators.
- Regulation and Efficiency of electrical machines.
- Speed Torque characteristics of Separately excited DC motor.


Unit - 5

Electrical Installation.

- Basic electrical Installation are SFU (switch fuse Unit)
- MCB's (Main circuit Breakers)
- Types of Wires and cables.
- Types of Batteries.
- Power factor Improvement.

Resistance in Series and Parallel Connection

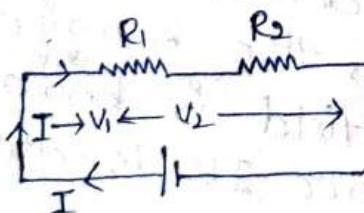1. Resistance in series : In this case the series connection of resistance in a circuit the same current flowing through all the elements shown in fig



from the above circuit based on the $V = V_1 + V_2$ (according to ohm's law $V = IR$)

$$IR = IR_1 + IR_2$$

$$IR = I(R_1 + R_2)$$

Now for 'n' turns in resistance connection in series $R = R_1 + R_2$
 $R_{eq} = R_1 + R_2 + R_3 + \dots + R_n$

It is denoted by "P". The units of the resistivity is "ohm-meter" ($\Omega \cdot m$)

$$P = \frac{R A}{l}$$

→ Conductivity : It is defined as the reciprocal of resistivity is known as conductivity. It is denoted by "σ". The units of the conductivity is " $\Omega^{-1} \text{ m}^{-1}$ " (or) $\text{v} \cdot \text{m}$

$$\sigma = 1/P$$

→ Conductor : It is defined as the material in which allows the flow of electrons is known as conductor. The example of the conductor are Aluminium, Copper, Silver.

→ Insulator : The material in which does not allow the flow of electrons is known as the Insulator. The example of Insulator are Rubber, Wood, Plastic.

→ Semi-Conductor : The material as the electric conductivity between conductor and Insulator is known as the semi-conductor.

→ Node : It is defined as the terminal of any branch of network (or) Inter Connection of two or more branches of network is known as node.

www.android.universityupdates.in / www.universityupdates.in / www.ios.universityupdates.in

→ Power : It is defined as the product of Voltage and current is known as Power. It is denoted by "P". The units of the power are "Watts."

$$P = VI$$

Limitations of Ohm's Law :


- * It is applicable to all metallic conductors such as silver, copper, aluminium.
- * It is not applicable all electrical circuit elements such as vacuum cleaner and transistors.

→ Conductance : It is defined as the reciprocal of resistance is known as a conductance.

It is denoted by G . The units of conductance is Ω^{-1} (or) S (ohm)

$$G = 1/R$$

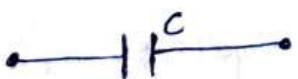→ Resistivity : It is defined as the resistance of the material as the unit length and unit area of cross section is known as the resistivity. 'c' The units of capacitance is microfarad (μF)



* → Ohm's law :

Statement : At constant temperature the flow of current in a electrical circuit is directly proportional

to Voltage and inversely proportional to resistance.

$$I \propto V/R$$

$$I = V/R \Rightarrow V = IR$$

$$R = V/I$$

→ Voltage : It is defined as the total amount of workdone to charge is known as a voltage. It is also known as potential difference. It is denoted by 'V'. The units of voltage is "Volts (V)"

→ Current : It is defined as the flow of electrons in a closed path is known as a current.

(or)

The rate of change of charge with respect to time.

$$i = \frac{dq}{dt}$$

Its unit is "Ampere (A)"

Semiconductor:

The examples of Semiconductor are Germanium and Silicon.

DC - Circuits

Introduction of Basic Electrical Elements.

→ **Resistor:** It is defined as the element which opposes the current. The resistance of the conductor is directly proportional to unit length and inversely proportional to unit area of cross section.

The mathematical expression of resistance are

$$R \propto l/a$$

$$R = \rho l/a$$

ρ = Resistivity of conductor

l = Unit length

a = Unit area of cross section.

The resistance is denoted by 'R' and the units of resistance is ohm's (Ω)

→

→ **Inductance:** It is defined as the elements in which the energy stored in magnetic field is known as the Inductance. It is denoted by "L".

The units of Inductance is "Henry (H)"

→

→ **Capacitance:** It is defined as the elements in which the energy stored in electric field is known as the capacitance. It is denoted by "C".

(Q-V and Zeta of parallel plane)


$$C = \frac{Q}{V}$$

$$C = \epsilon A/d$$

$$C = \epsilon_0 \epsilon_r A/d$$

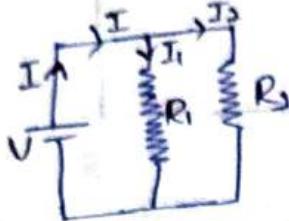2. Resistance in Parallel:

In this case of parallel connection in electric circuit the voltage across same elements. The electric circuit shown in fig.



the above circuit based on the eqn $I = I_1 + I_2$
(according to Ohm's law $I = V/R$)

$$I = I_1 + I_2$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\sqrt{\left(\frac{1}{R}\right)} = \sqrt{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)}$$


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \rightarrow \frac{1}{R} = \frac{R_1 + R_2}{R_1 R_2}$$

By the 'n' no. of turns in resistance

connected in parallel. The eqn are

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

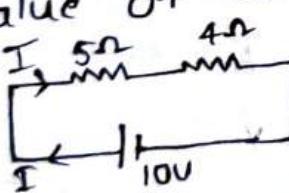Problems:
* find the value of current as shown in diagram.




Sol: $R = R_1 + R_2$

$$R = 5 + 4$$

$$R = 9 \Omega$$

$$R_{eq} = 9 \Omega$$

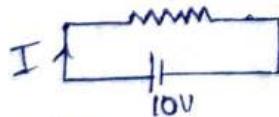


$$V = IR$$

$$I = V/R$$

$$I = 10/9$$

$$I = 1.1 A$$

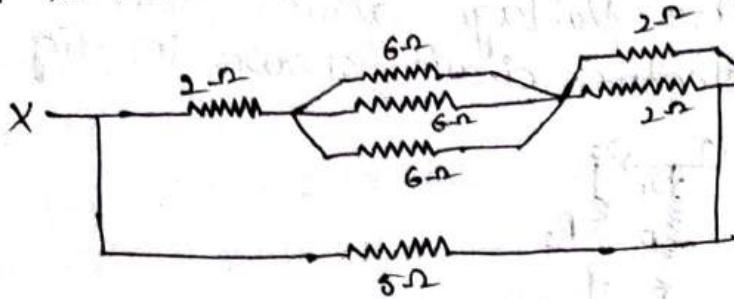3) find the equivalence resistance at the terminals
of X & Y.



Sol: Given

$$\text{For hexagon: } \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{6} + \frac{1}{6}$$

$$\frac{1}{R} = \frac{3}{6}$$

$$\frac{1}{R} = \frac{1}{2}$$


$$R = 2\Omega$$

$$\text{For 2 ohm bridge: } \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{1}{2} + \frac{1}{2}$$

$$\frac{1}{R} = \frac{2}{2}$$


$$R = 1\Omega$$

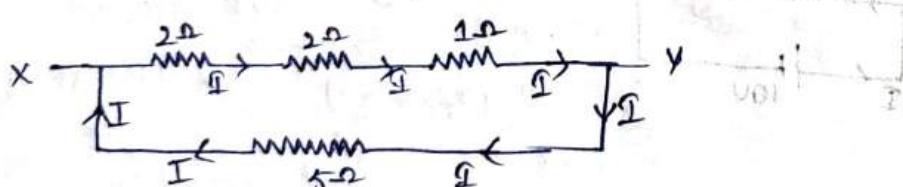

$$R = R_1 + R_2 + R_3$$

$$= 2 + 2 + 1$$


$$R = 5\Omega$$

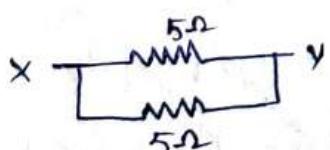


$$R = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow \frac{5 \times 5}{5 + 5} \Rightarrow \frac{25}{10}$$

$$\therefore R_{eq} = 2.5\Omega$$

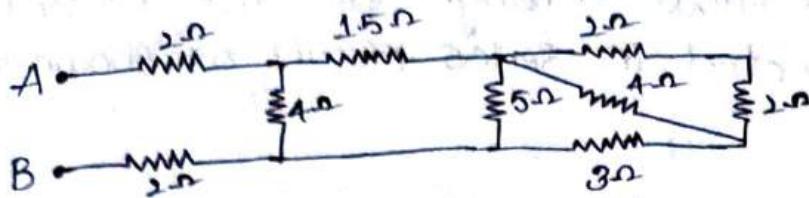3) find the equivalent resistance between two terminals A & B the circuit shown in below.



Sol:

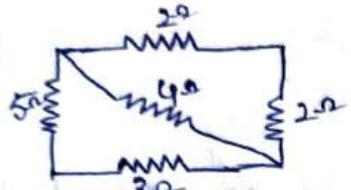


$$R = R_1 + R_2$$

$$= 2 + 2$$

$$R = 4\Omega$$


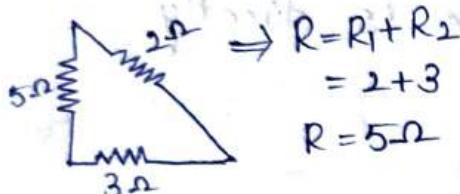
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$\Rightarrow R = R_1 + R_2$$

$$= 2 + 3$$

$$R = 5\Omega$$

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{4}$$

$$\frac{1}{R} = \frac{2}{4}$$

$$RV = 2\Omega$$

$$\begin{aligned} &\text{Simplification of the circuit by combining resistors 5Ω and } 3\Omega \text{ in parallel.} \\ &\Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \\ &\frac{1}{R} = \frac{1}{5} + \frac{1}{3} \\ &\frac{1}{R} = \frac{3+5}{15} \\ &\frac{1}{R} = \frac{8}{15} \\ &R = 2.5\Omega \end{aligned}$$

$$\begin{aligned} &\text{Simplification of the circuit by combining resistors 1.5Ω and } 2.5\Omega \text{ in parallel.} \\ &\Rightarrow R = R_1 + R_2 \end{aligned}$$

$$R = 1.5 + 2.5$$

$$R = 4\Omega$$

$$\begin{aligned} &\text{Simplification of the circuit by combining resistors 4Ω and } 4Ω \text{ in parallel.} \\ &\Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \frac{1}{R} = \frac{1}{4} + \frac{1}{4} \\ &\frac{1}{R} = \frac{2}{4} \\ &R = \frac{4}{2} \Rightarrow R = 2\Omega \end{aligned}$$

$$\begin{aligned} &\text{Simplification of the circuit by combining resistors 2Ω and } 2Ω \text{ in parallel.} \\ &\Rightarrow R = R_1 + R_2 \end{aligned}$$

$$= 2 + 2$$

$$R = 4\Omega$$


$$\begin{aligned} &\text{Simplification of the circuit by combining resistors 4Ω and } 2Ω \text{ in parallel.} \\ &\Rightarrow R = R_1 + R_2 \end{aligned}$$

$$= 4 + 2$$

$$R = 6\Omega$$

Inductance in Series Connection:

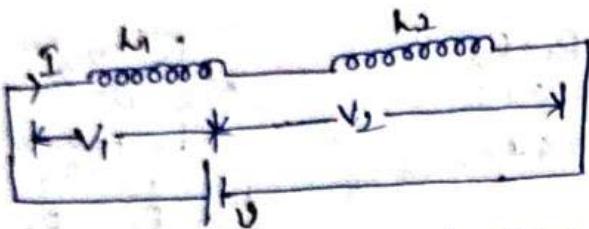In this case of Series connection the same current will flow through all the elements which are connected in Series circuit as shown in fig.



The voltage and current relationship between in the Inductance and the rate of change of current with respect to time is directly proportional to Voltage

$$V \propto \frac{di}{dt}$$

$$V = L \frac{di}{dt} \quad \text{--- (1)}$$

$$i = \frac{1}{L} \int V dt \quad \text{--- (2)}$$

$$\left[\because \frac{d}{dx} (\text{some}) = f(\text{some}) dx \right]$$

$$di = \frac{1}{L} V dt$$

$$\int di = \frac{1}{L} \int V dt$$

$$i = \frac{1}{L} \int V dt$$

from the above circuit based on the equation

$$V = V_1 + V_2$$

According to Voltage-Current relationship between Inductance ($V = L \frac{di}{dt}$)

$$V = V_1 + V_2$$

$$L \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

$$L \frac{di}{dt} = \frac{di}{dt} (L_1 + L_2)$$

$$i = i_1 + i_2$$


$$\therefore L_{eq} = L_1 + L_2 + L_3 + \dots + L_n$$

\therefore The "n" no. of turns inductance are connected in Series the equivalent inductance equation are

$$L_{eq} = L_1 + L_2 + \dots + L_n$$

Inductance in Parallel Connection:

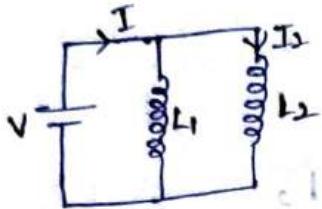In this case of llel connection the same voltage across each branch from the circuit as shown in fig.



from above circuit based on the equation

$$I = I_1 + I_2$$

According to voltage-current relationship between Inductance ($\because i = \frac{1}{L} \int v dt$)

$$I = I_1 + I_2$$


$$\frac{1}{L} \int v dt = \frac{1}{L_1} \int v dt + \frac{1}{L_2} \int v dt$$

$$\frac{1}{L} \int v dt = \int v dt \left(\frac{1}{L_1} + \frac{1}{L_2} \right)$$

$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$$


\therefore the no. of turns connected in llel the equivalent inductance equation is
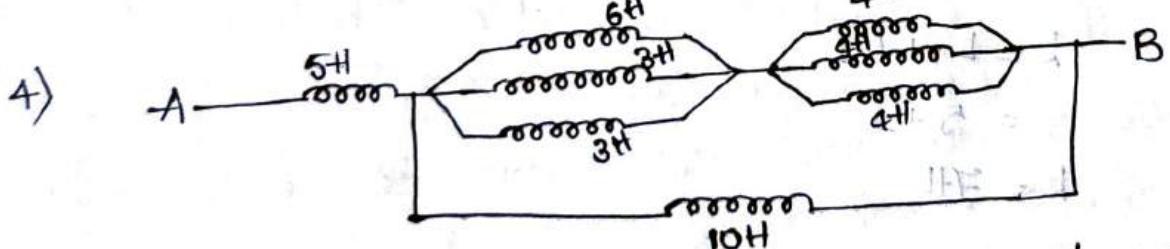
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$



find the equivalent inductance between the two terminals A & B as shown in fig

Sol:

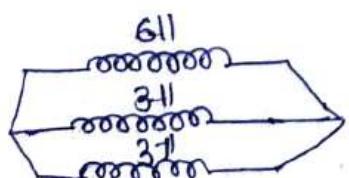


$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$= \frac{1}{6} + \frac{1}{3} + \frac{1}{3}$$

$$= \frac{1+2+2}{6} \Rightarrow \frac{5}{6}$$

$$L = 1.083H$$

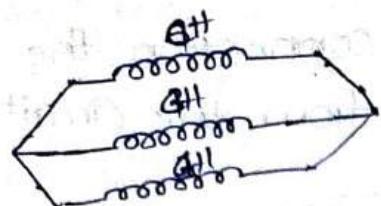

$$\frac{1}{L} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{L} = \frac{1}{4} + \frac{1}{4} + \frac{1}{4}$$

$$\frac{1}{L} = \frac{3}{4}$$

$$L = 1.33\Omega$$

$$\frac{1.2}{R_1} + \frac{1.3}{R_2} \Rightarrow L = R_1 + R_2$$

$$= 1.2 + 1.3$$

$$L = 2.5\Omega$$

connected opposition tension - opposition at position A

$$\frac{2.5}{R_1} + \frac{10}{R_2} \Rightarrow \frac{1}{L} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$= \frac{1}{2.5} + \frac{1}{10}$$

$$\frac{1}{L} = \frac{10}{25} + \frac{1}{10}$$

$$\frac{1}{L} = \frac{100+25}{250}$$

$$\frac{1}{L} = \frac{125}{250}$$
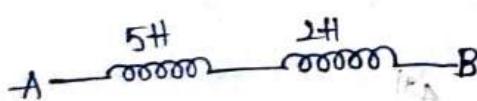
$$L = \frac{250}{125} \Rightarrow L = 2\Omega$$



$$L = R_1 + R_2$$

$$= 5 + 2$$

$$L = 7\Omega$$


With connected opposition tension - opposition

at position B on resistor R2 & A on resistor R1

Opposition at position B


Opposition at position A

Opposition at position B

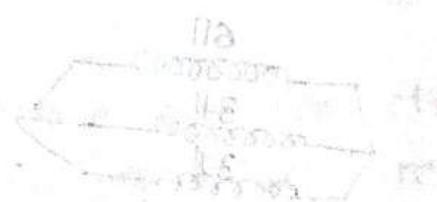

Capacitance in Series:

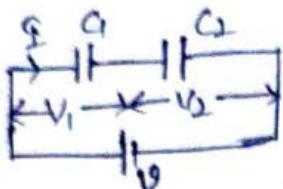In this case of Series Connection Same Current will flow through all the elements which are connected in Series as shown in fig.



The Voltage and current relationship between capacitance. The current is directly proportional to rate of change of voltage with respect to time.

$$i \propto \frac{dv}{dt}$$

$$i = C \frac{dv}{dt}$$

$$V = \frac{1}{C} \int i dt$$

from above circuit based on the eqn $V = V_1 + V_2$
According to voltage and current relationship b/w
capacitance.

$$V = \frac{1}{C} \int i dt$$

$$V = V_1 + V_2$$

$$\frac{1}{C} \int i dt = \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt$$

$$\frac{1}{C} \int i dt = \int i dt \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$


$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

∴ for 'n' no. of turns capacitance are connected in Series the equivalent capacitance eqn. is

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

Capacitance in Parallel:

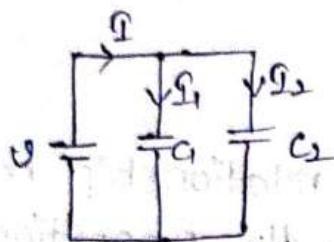In this case of parallel connection the same voltage across each branch from circuit which are connected in parallel as shown in fig.



from the circuit based on the eqn. $I = I_1 + I_2$
According to Voltage and Current relationship b/w
capacitance $(i = C \frac{du}{dt})$

$$I = I_1 + I_2$$

$$C \frac{du}{dt} = C_1 \frac{du}{dt} + C_2 \frac{du}{dt}$$


$$C \frac{du}{dt} = \frac{du}{dt} (C_1 + C_2)$$

$$C = C_1 + C_2$$



∴ for 'n' no. of turns capacitance are connected in parallel the equivalent capacitance is

$$C_{eq} = C_1 + C_2 + \dots + C_n$$

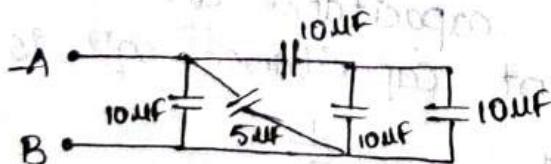5) find the equivalent capacitance between the terminal A & B as shown in fig.




Sol:

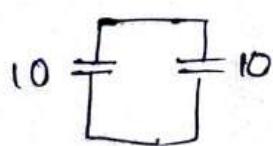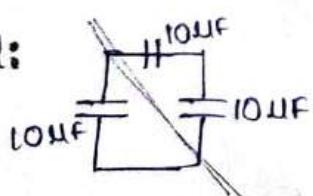

$$C = C_1 + C_2 \\ = 10 + 10$$

$$C = 20 \mu F$$

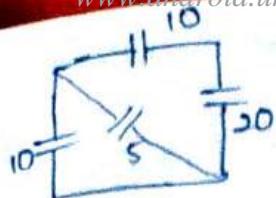

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C} = \frac{1}{10} + \frac{1}{20}$$

$$\frac{1}{C} = \frac{2+1}{20} \Rightarrow \frac{3}{20}$$

$$C = \frac{20}{3}$$


$$C = 6.6$$



$$C = C_1 + C_2$$

$$= 5 + 6.6$$

$$C = 11.6 \mu F$$

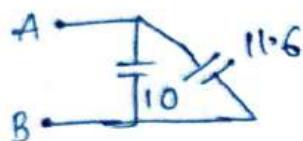

$$C = C_1 + C_2$$



$$C = 10 + 11.6$$

$$C = 21.6 \mu F$$

$$\therefore C_{eq} = 21.6 \mu F$$

6) find the equivalent capacitance b/w the terminals A & B.

Sol:

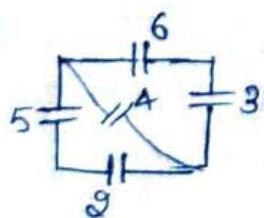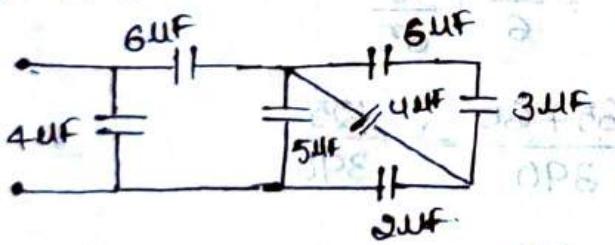

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$


$$= \frac{1}{6} + \frac{1}{3}$$

$$\frac{1}{C} = \frac{1+2}{6}$$


$$\frac{1}{C} = \frac{3}{6} = \frac{1}{2}$$

$$\frac{1}{C} = \frac{1}{2}$$

$$C = 2 \mu F$$

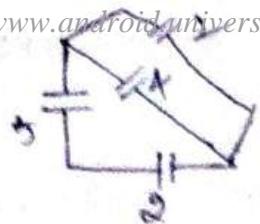

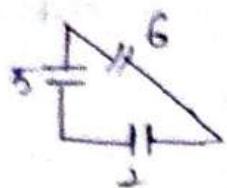
$$\begin{aligned} C &= C_1 + C_2 \\ &= 4 + 2 \\ C &= 6 \mu F \end{aligned}$$



$$\begin{aligned} \frac{1}{C} &= \frac{1}{C_1} + \frac{1}{C_2} \\ \frac{1}{C} &= \frac{1}{6} + \frac{1}{2} \\ \frac{1}{C} &= \frac{1+3}{6} = \frac{4}{6} \end{aligned}$$

$$\frac{1}{C} = \frac{2}{3}$$


$$C = 1.5 \mu F$$

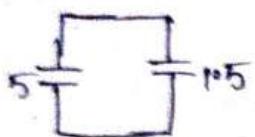

$$C = C_1 + C_2$$

$$C = 1.5 + 5$$

$$C = 6.5 \mu F$$

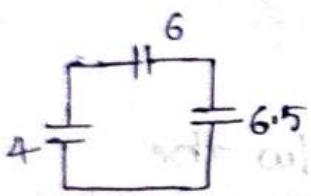

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$


$$\frac{1}{C} = \frac{1}{6} + \frac{1}{6.5}$$

$$\frac{1}{C} = \frac{1}{6} + \frac{10}{65}$$

$$\frac{1}{C} = \frac{65+60}{390} \Rightarrow \frac{125}{390}$$

$$C = \frac{390}{125}$$

$$C = 3.12 \mu F$$

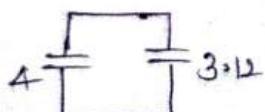

$$C = C_1 + C_2$$

$$C = 4 + 3.12$$

$$C = 7.12 \mu F$$

$$\therefore C_{eq} = 7.12 \mu F$$

Power and Energy relationship between (R, L & C)

Resistance: The power observed by the resistance are given by $P = VI$

According to ohm's law resistance are two conditions $[V = IR, I = V/R]$

$$P = VI$$

$$P = IR(I)$$

$$\boxed{P = I^2 R}$$

$$P = VI$$

$$P = V\left(\frac{V}{R}\right) \Rightarrow \boxed{P = \frac{V^2}{R}}$$

→ The energy observed by the resistance are given by

$$W = \int P dt$$

According to the ohm's law resistance are two conditions $[V = IR, I = V/R]$

$$W = \int P dt$$

$$W = P \int dt$$

$$W = Pt$$

$$W = VI t$$

$$W = IR(It)$$

$$\boxed{W = I^2 R t}$$

$$W = Pt$$

$$W = VIt$$

$$W = V\left(\frac{V}{R}\right)t$$

$$\boxed{W = \frac{V^2 t}{R}}$$

$$PV = q \quad \text{pd. resistive energy}$$

Inductance: The Power observed by the Inductance are given by $P = VI$

According to Voltage is directly proportional to the rate of change of current with respect to time.

$$V \propto \frac{di}{dt}$$

where

$$V = L \frac{di}{dt}$$

$$P = VI$$

$$P = L \frac{di}{dt} \quad (i)$$

$$P = L i \frac{di}{dt}$$

→ The energy observed by the inductance are given by

$$w = \int P dt$$

$$w = \int V I dt$$

According to voltage is directly proportional to the rate of change of current w.r.t time

$$V \propto \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$

$$w = \int P dt$$

$$w = \int V I dt$$

$$w = \int L \cdot \frac{di}{dt} I dt$$

$$w = L \int i di$$

$$w = \frac{L i^2}{2}$$

Capacitance : The power observed by the capacitance are given by $P = V I$

According to current is directly proportional to the rate of change of Voltage w.r.t. time

$$i \propto \frac{dv}{dt}$$

$$i = C \frac{dv}{dt}$$

$$P = V I$$

$$P = C V \frac{du}{dt}$$

→ The energy observed by the capacitance are given by $\omega = \int P dt$
 $\omega = \int VI dt$

According to current is directly proportional to the rate of change of voltage w.r.t. time

$$\omega = \int I C \frac{du}{dt} dt$$

$$\omega = C \int V d\vartheta$$

$$\boxed{\omega = C \frac{V^2}{2}}$$

Component	Relationship	I	P	E
R	$V = IR$	$I = V/R$	$P = I^2 R$ (cor) $P = \frac{V^2}{R}$	$\omega = I^2 R t$ (cor) $\omega = \frac{V^2 t}{R}$
L	$V = L \cdot \frac{di}{dt}$	$i = \frac{1}{L} \int V dt$	$P = L i \frac{di}{dt}$	$\omega = \frac{Li^2}{2} t$
C	$V = \frac{1}{C} \int i dt$	$i = C \frac{d\vartheta}{dt}$	$P = C u \frac{du}{dt}$	$\omega = \frac{Cu^2}{2}$

* Network Elements :

The network elements are classified into five types. They are:

- Active and Passive element
- Unilateral and Bilateral element
- Linear and Non-linear element
- Lumped and distributed element
- Time Variant and Time in-Variant element

i) Active and Passive element:

The element which can deliver energy

is known as a Active element

ex: Energy sources (current & voltage)

The element which consume the energy either receiving (or) stores the energy is known as Passive element

ex: Resistance (R), Inductance (L), Capacitance (C)

ii) Unilateral and Bilateral:

(Unilateral elements offers low resistance for the flow of current in one direction and high resistance for the flow of current in opposite direction is known as unilateral element.) They have different voltage and current relationship for the two possible direction of current.

ex: Semiconductor devices and diodes.

→ Bilateral elements offers same resistance for the flow of current either direction is known as bilateral element. They have same voltage and current relationship for the two possible direction of current.

ex: Resistance, Inductance, Capacitance.

iii) Linear and Non-linear element:

A circuit elements said to be linear if it is satisfy the relationship b/w Voltage and current (Ohm's law)

$$V \propto I$$

$$V = IR$$

$$V \propto \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$

$$i \propto \frac{dv}{dt}$$

$$i = C \frac{dv}{dt}$$

↳ Resistance, Inductance and Capacitance:

↳ Circuit elements said to be non-linear if it doesn't satisfy the relationship b/w voltage and current is known as non-linear elements.

↳ Diodes and Thermometer:

Lumped and Distributed elements:

The elements which are physically separable elements is known as a lumped elements.

Inductance and Capacitance:

↳ The elements which are physically un-separable elements is known as a distributed elements.

↳ A transmission line has distributed resistance

Inductance and capacitance along its length.

Time Variant and Time Invariant Elements:


If the parametric of the network element do not vary with time is known as time invariant elements.

→ If the parametric of the network elements do vary with time is known as time variant elements.


→ Normally, we consider network elements are linear, Time invariant and lumped elements.

Voltage division Rule:

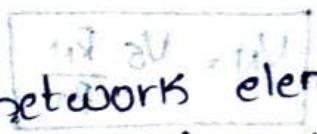A Series circuit resistors acts as a Voltage division since, the same current flowing in each resistance value. The voltage drops are directly proportional to the each value of the resistances.



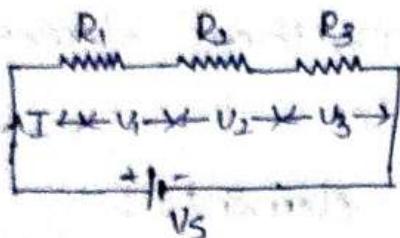The resistors are connected in Series as shown in figure using principle difference of voltage are obtained from single source.



from the circuit based on the eqn $V = \frac{Vs}{R_T}$

Where $R_T = R_1 + R_2 + R_3 \dots$ total resistance connected in Series.

$$V = IR$$

$$V_1 = IR_1$$

$$V_1 = \frac{Vs}{R_T} R_1$$

$$V_1 = Vs \frac{R_1}{R_T}$$

$$V_2 = Vs \frac{R_2}{R_T}$$

$$V_3 = Vs \frac{R_3}{R_T}$$

$$V_N = Vs \frac{R_N}{R_T}$$

The general eqn for voltage division rule.

Where $V_N =$ Voltage across N resistor


$R_N =$ Resistance across voltage value is determined

$R_T =$ The total resistance are connected in Series.

★ Current division Rule:

In Parallel circuit the current is divided into all branches the parallel circuit acts as a current divider. The total amount of current is divided into branch current.

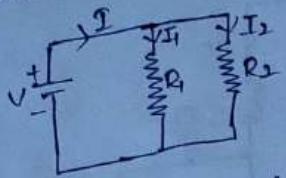according to each value of resistance.
Let. Consider the llcl circuit as shown in fig



from the circuit the value of current I_1 & I_2 ,
are given by $I_1 = V/R_1$, $I_2 = V/R_2$

$$\text{Total resistance } R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{Total Current } I = V/R_T \Rightarrow I = \frac{I_1 R_1}{R_T}$$

$$I = I_1 \times \frac{R_1 + R_2}{R_2}$$

$$I_1 = I \times \frac{R_2}{R_1 + R_2}$$

$$\text{By } I_2 = I \times \frac{R_1}{R_1 + R_2}$$

General eqn of
current division
rule


$$I_N = I \times \frac{R_T}{R_T + R_N}$$

Where,


I_N = Current in n^{th} resistor

R_N = Resistance of n^{th} term.

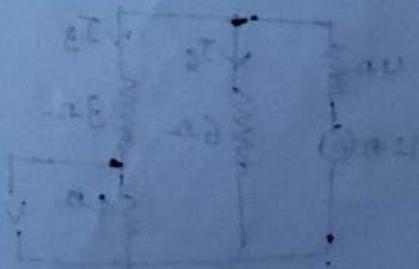R_T = Resistance are llcl branches of
 n^{th} term.



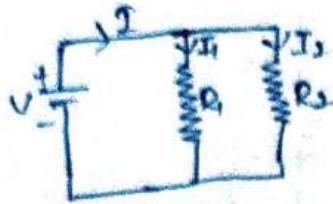according to each value of resistance.
Let. Consider the llcl circuit as shown in fig



from the circuit the value of current I_1 & I_2 ,
are given by $I_1 = V/R_1$, $I_2 = V/R_2$

$$\text{Total resistance } R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{Total Current } I = V/R_T \Rightarrow I = \frac{I_1 R_1}{R_T}$$

$$I = \frac{I_1 R_1}{R_1 R_2} \times R_1 + R_2$$

$$I = I_1 \times \frac{R_1 + R_2}{R_2}$$

$$I_1 = I \times \frac{R_2}{R_1 + R_2}$$

$$\text{Hence } I_2 = I \times \frac{R_1}{R_1 + R_2}$$

General eqn of
current division
rule

$$I_N = I \times \frac{R_T}{R_T + R_N}$$


Where,
 I_N = Current in n^{th} resistor

R_N = Resistance of n^{th} term.

R_T = Resistance of all parallel branches of
circuit or sum of all parallel resistances.



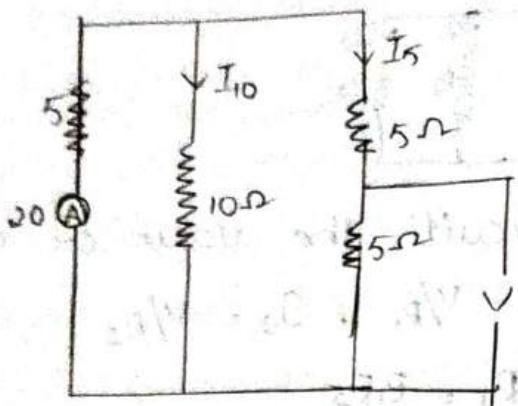Q) Determine the current in 10Ω resistor and find the value of voltage in the circuit as shown in fig.



$$\text{Sol: } I_1 = I \times \frac{R_2}{R_1 + R_2}$$

$$R_T = 5 + 5 = 10\Omega$$

$$I_{10} = 20 \times \frac{10}{10+10}$$

$$I_{10} = 20 \times \frac{10}{20}$$

$$\boxed{I_{10} = 10 \text{ A}}$$

$$I_5 = I \times \frac{R_1}{R_1 + R_2}$$

$$= 20 \times \frac{10}{10+10}$$

$$= 20 \times \frac{10}{20}$$


$$\boxed{I_5 = 10 \text{ A}}$$

$$V = I_5 R$$

$$= 10 \times 5$$

$$= 50 \text{ V}$$

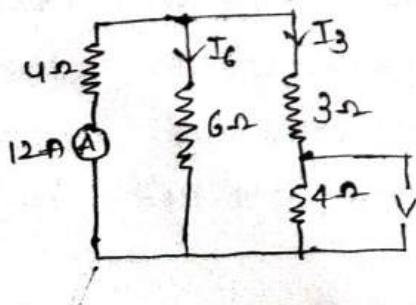* Q) Determine the current in 6Ω resistor and find the value of voltage in the circuit as shown.



$$\text{Soln} \quad I_6 = I \times \frac{R_2}{R_1 + R_2}$$

$$R_T = 6 + 3 \\ = 9$$

$$I_6 = 12 \times \frac{7}{6+7} \\ = 12 \times \frac{7}{13}$$

$$I_6 = \frac{84}{13}$$

$$I_6 = 6.4 \text{ A}$$

$$I_3 = I \times \frac{R_1}{R_1 + R_2}$$

$$= 12 \times \frac{6}{6+7}$$

$$= 12 \times \frac{6}{13}$$


$$I_3 = \frac{72}{13}$$

$$I_3 = 5.5 \text{ A}$$


$$V = I_3 R \\ = 5.5 \times 4$$

$$V = 22 \text{ V}$$

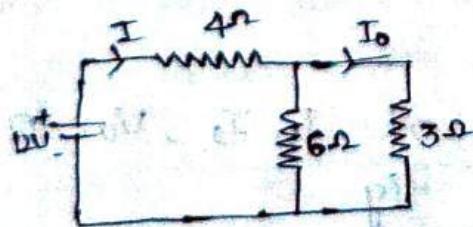- (Q) Using voltage and current division rule find the values of V_o, I_o in the circuit as shown in fig



Sol:

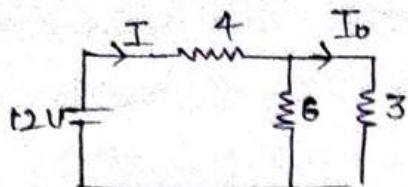


$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{3}$$

$$= \frac{1+2}{6}$$

$$= \frac{3}{6}$$

$$\frac{1}{R_{eq}} = \frac{1}{2}$$

$$R_{eq} = 2\Omega$$

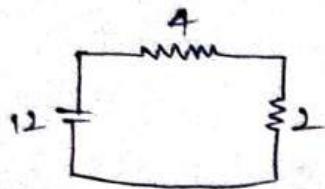

$$R_{eq} = R_1 + R_2$$

$$= 4 + 2$$

$$R_{eq} = 6\Omega$$

$$I = \frac{V}{R}$$

$$I = \frac{12}{6}$$

$$I = 2A$$

$$I_0 = I \times \frac{R_T}{R_T + R_N}$$

$$= 2 \times \frac{6}{6+3}$$

$$= 2 \times \frac{6^2}{9^3}$$

$$= \frac{4}{3}$$


$$I_0 = 1.3A$$

$$V_0 = I_0 R$$

$$= 1.3 \times 3$$

$$V_0 = 3.9V$$

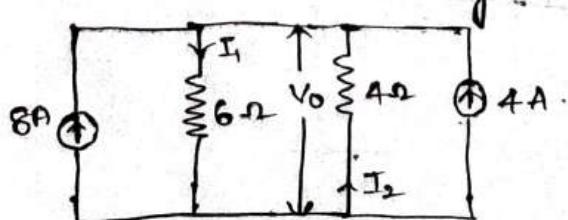- Q) Determine the value of I_1 , I_2 , V_0 in the circuit as shown in fig.



$$I = 8 + 4 = 12A$$

$$I_1 = I \times \frac{R_1}{R_1 + R_2}$$

$$I = 12 \times \frac{4}{4+6}$$

$$I = 12 \times \frac{4}{10}$$

$$I = \frac{48}{10}$$

$$\boxed{I_1 = 4.8A}$$

$$I_2 = I \times \frac{R_2}{R_1 + R_2}$$

$$I_2 = 12 \times \frac{6}{6+4}$$

$$= 12 \times \frac{6}{10}$$

$$\boxed{I_2 = 7.2A}$$


As the current I_2 is in Opposite direction then I_2 becomes "negative sign":

$$\boxed{I_2 = -7.2A}$$


$$V_o = I_1 \times R_1$$

$$= 4.8 \times 6$$

$$\boxed{V_o = 28.8V}$$

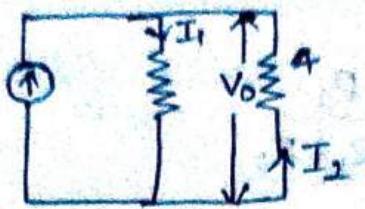

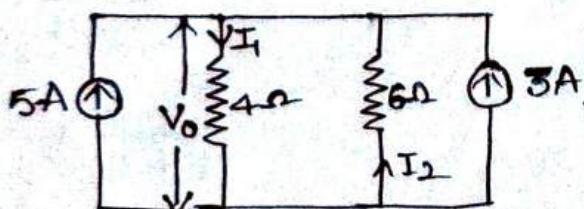- i) Determine the value of I_1 , I_2 , V_o in the circuit as shown in fig.



$$\underline{\underline{S \text{ Sol: } I = 5+3}}$$

$$I = 8A$$

$$I_1 = I \times \frac{R_1}{R_1 + R_2}$$

$$= 8 \times \frac{6}{4+6}$$

$$= 8 \times \frac{6}{10}$$

$$= \frac{48}{10}$$

$$\boxed{I_1 = 4.8A}$$

$$I_2 = I \times \frac{R_2}{R_1 + R_2}$$

$$= 8 \times \frac{4}{4+6}$$

$$= 8 \times \frac{4}{10}$$

$$= \frac{32}{10}$$

$$\boxed{I_2 = 3.2A}$$

As the current I_2 is opposite direction then I_2 becomes "negative sign":

$$\boxed{I_2 = -3.2A}$$


$$V_0 = I_1 \times R_1$$

$$= 4.8 \times 6$$

$$\boxed{V_0 = 28.8V}$$

(6)

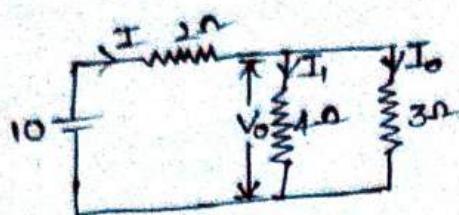a) Using Voltage and Current division rule find the values of V_o, I_o in the circuit as shown in fig.



$$\text{Sol: } \frac{1}{R_{\text{eq}}} = \frac{1}{4} + \frac{1}{3}$$

$$\frac{1}{R_{\text{eq}}} = \frac{3+4}{12} = \frac{8}{12}$$

$$\frac{1}{R_{\text{eq}}} = \frac{2}{3}$$

$$R_{\text{eq}} = \frac{3}{2}$$

$$\therefore R_{\text{eq}} = 1.5 \Omega$$

$$R_{\text{eq}} = R_1 + R_2$$

$$= 2 + 1.5$$

$$R_{\text{eq}} = 3.5 \Omega$$

$$I = \frac{V}{R}$$

$$= \frac{10}{3.5}$$



$$I = 2.8 \text{ A}$$

$$I_o = I \times \frac{R_T}{R_T \times R_N}$$

$$= 2.8 \times \frac{4}{4+3}$$

$$= 2.8 \times \frac{4}{7}$$

$$= \frac{11.2}{7}$$

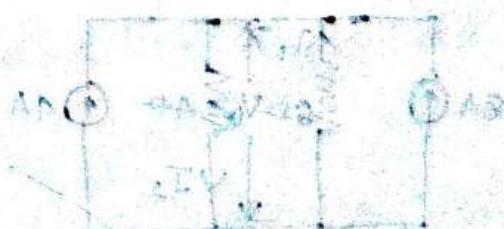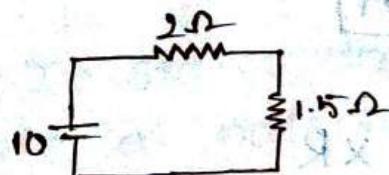

$$I_0 = 1.6 \text{ A}$$

$$V_0 = I_0 \times R \\ = 1.6 \times 4$$

$$V_0 = 6.4 \text{ V}$$

$$I_0 = 1.6 \text{ A}$$

$$I_1 = I \times \frac{R_1}{R_1 + R_N}$$

$$= 2.8 \times \frac{3}{3+4}$$

$$= 2.8 \times \frac{3}{7}$$


$$I_1 = 1.2 \text{ A}$$

$$V_0 = I_1 \times R$$

$$= 1.2 \times 4$$

$$V_0 = 4.8 \text{ V}$$

(6)

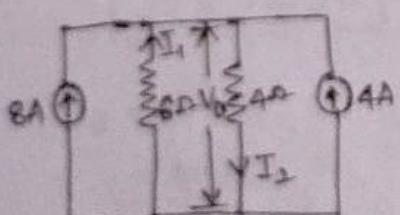

$$\underline{\text{Sol:}} \quad I = 8 - 4$$

$$I = 4 - 2$$

$$I_1 = I \times \frac{R_1}{R_1 + R_2} \\ = 4 \times \frac{4}{6+4}$$

$$I_1 = 4 \times \frac{4}{10} \\ = \frac{16}{10}$$

$$I_1 = 1.6 \text{ A}$$

Kirchoff's law
Kirchoff's

1. Kirchoff's
2. Kirchoff's
- * Kirchoff's algebraic sum 'zero' is K

The sum of equal to sum is known as

Eg: Application shown

$$I_0 = 1.6A$$

$$V_0 = I_0 \times R$$

$$= 1.6 \times 4$$

$$V_0 = 6.4V$$



$$I_0 = 1.6A$$

$$I_1 = I \times \frac{R_T}{R_T + R_N}$$

$$= 2.8 \times \frac{3}{3+4}$$

$$= 2.8 \times \frac{3}{7}$$


$$I_1 = 1.2A$$

$$V_0 = I_1 \times R$$

$$= 1.2 \times 4$$

$$V_0 = 4.8V$$

(Q)

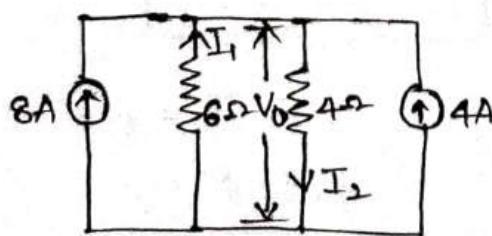

$$\text{Sol: } I = 8 - 4$$

$$I = 4A$$

$$I_1 = 1.2A$$

$$I_1 + I_2 = 4A$$

$$I_1 + I_2 = 4A$$

$$I_1 + I_2 = 4A$$

$$\frac{V_0}{R} = I_1$$

$$\frac{V_0}{4} = 1.2$$

$$V_0 = 4.8V$$

$$I_1 = \frac{V_0}{R} = 1.2$$

$$4.8 \times 1 = 4.8$$

$$I_1 = \frac{V_0}{R} = 1.2$$

$$I_1 = I \times \frac{R_2}{R_1 + R_2}$$

$$= 4 \times \frac{4}{6+4}$$

$$I_1 = 4 \times \frac{4}{10}$$

$$= \frac{16}{10}$$

$$I_1 = 1.6 \text{ A}$$

$$I_2 = I \times \frac{R_1}{R_1 + R_2}$$

$$= 4 \times \frac{6}{6+4}$$

$$= 4 \times \frac{6}{10}$$

$$= \frac{24}{10}$$

$$I_2 = 2.4 \text{ A}$$

$$V_o = I_1 R_1$$

$$V_o = -1.6 \times 6$$

$$V_o = -9.6 \text{ V}$$

Kirchoff's law:

Kirchoff's law is classified into two types:

1. Kirchoff's current law [KCL]
2. Kirchoff's voltage law [KVL]


1st Kirchoff's Current law : It states that the algebraic sum of currents at node is equal to 'zero' is known as KCL.

(or)

The sum of the current entering at node is equal to sum of the current leaving at node is known as KCL.

Ex: Application of KCL at node is given as shown in fig.

$$i_1 + i_2 + i_3 + i_4 + i_5 = 0$$

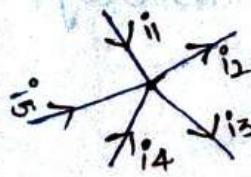

$$i_1 - i_2 - i_3 + i_4 + i_5 = 0$$


The Sum of the current entering at node equal to sum of the current leaving at node.

$$i_1 + i_4 + i_5 = i_2 + i_3$$

Kirchhoff's Voltage Law:

It states that the algebraic sum of the potential difference (or) voltage around the closed circuit is equal to 'Zero' is known as KVL.

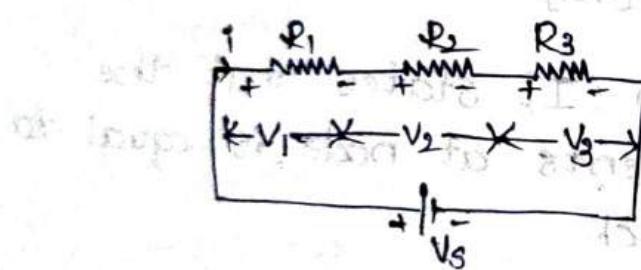The example of electric circuit resistance are connected in series as shown in fig. The voltage source are having two ends (neg, pos) The voltage source passing through +ve end the voltage drops are '-ve' and the voltage source are passing through -ve end the voltage drops are '+ve'.



from the circuit based on the eqn's in voltage source passing through +ve end is given as:

$$V_s - V_1 - V_2 - V_3 = 0$$

$$V_s = V_1 + V_2 + V_3$$


The voltage source passing through -ve end is given as

$$-V_s + V_3 + V_2 + V_1 = 0$$

$$V_s = V_1 + V_2 + V_3$$

Prblm:

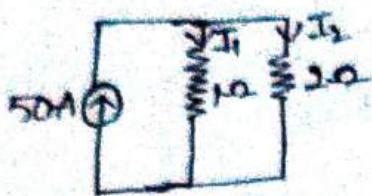- (a) By using KCL determine the values of I_1, I_2, V in the circuit shown in fig.



Sol: Sum of the current entering at node = Sum of the current leaving at node.

$$I = I_1 + I_2$$

$$50 = \frac{V}{1} + \frac{V}{2}$$

$$50 = \frac{2V + V}{2}$$

$$100 = 3V$$

$$V = \frac{100}{3}$$

$$V = 33.33$$

$$I_1 = \frac{V}{1} \Rightarrow \frac{33.33}{1}$$

$$I_1 = 33.33$$

$$I_1 = \frac{V}{1}, I = \frac{V}{2}$$

$$I_2 = \frac{V}{2} \Rightarrow \frac{33.33}{2}$$


$$I_2 = 16.66A$$

$$I = I_1 + I_2$$

$$50 = 33.33 + 16.66$$

$$50 \approx 49.99$$

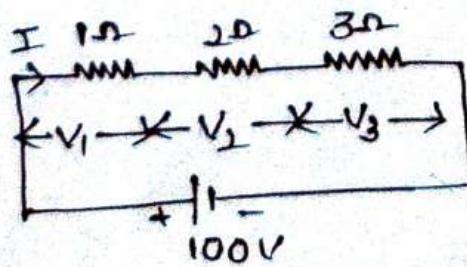- (b) By using KVL determine the values of V_1, V_2, V_3 and I in the circuit shown in fig.



Sol: $V = IR$

$$V = V_1 + V_2 + V_3$$

$$V = IR_1 + IR_2 + IR_3$$

$$100 = I(R_1 + R_2 + R_3)$$

$$100 = I(1+2+3)$$

$$100 = I(6)$$

$$I = \frac{100}{6}$$

$$\boxed{I = 16.66A}$$

$$V_1 = IR_1$$

$$V_1 = 16.66(1)$$

$$\boxed{V_1 = 16.66V}$$

$$V_2 = IR_2$$

$$V_2 = 16.66(2)$$

$$\boxed{V_2 = 33.32V}$$

$$V_3 = IR_3$$

$$V_3 = 16.66(3)$$

$$\boxed{V_3 = 49.98V}$$

$$V = V_1 + V_2 + V_3$$


$$V = 16.66 + 33.32 + 49.98$$

$$V = 99.96$$

$$100 \approx 99.96$$

Homework Problems

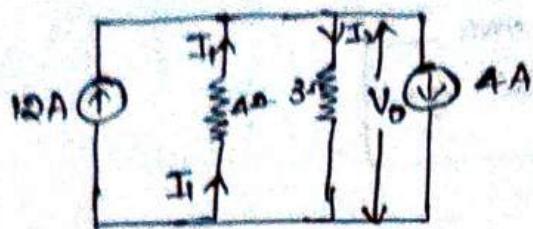→ Determine the value of I_1 , I_2 , V_o in the circuit as shown in fig.



$$\text{Sol: } \mathfrak{I} = 12 - 4$$

$$\mathfrak{I} = 8 \text{ A}$$

$$I_1 = \mathfrak{I} \times \frac{R_2}{R_1 + R_2}$$

$$= 8 \times \frac{3}{4+3}$$

$$= 8 \times \frac{3}{7}$$

$$= \frac{24}{7}$$

$$I_1 = 3.4$$

As the current I_1 is in Opposite direction then \mathfrak{I}_1 becomes "negative sign."

$$\mathfrak{I}_1 = -3.4$$

$$I_2 = \mathfrak{I} \times \frac{R_1}{R_1 + R_2}$$

$$= 8 \times \frac{4}{4+3}$$

$$= 8 \times \frac{4}{7}$$

$$= \frac{32}{7}$$


$$I_2 = 4.5$$

$$V_o = I_1 \times R_1$$

$$= -3.4 \times 3$$

$$V_o = -10.2$$

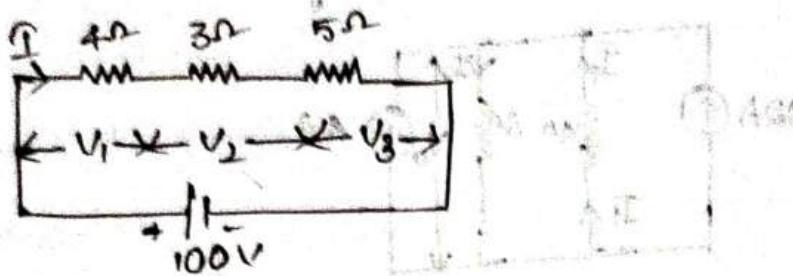Q) By using KVL determine the values of V_1, V_2, V_3 and I in the circuit as shown in fig.



Sol: $V = IR$

$$V = V_1 + V_2 + V_3$$

$$V = IR_1 + IR_2 + IR_3$$

$$V = I(R_1 + R_2 + R_3)$$

$$V = I(4 + 3 + 5)$$

$$100 = I(12)$$

$$I = \frac{100}{12}$$

$$I = 8.3 A$$

$$V_1 = IR_1$$

$$= 8.3(4)$$

$$V_1 = 33.2 V$$

$$V_2 = IR_2$$

$$= 8.3(3)$$

$$V_2 = 24.9 V$$

$$V_3 = IR_3$$

$$= 8.3(5)$$

$$V_3 = 41.5 V$$


$$V = V_1 + V_2 + V_3$$

$$= 33.2 + 24.9 + 41.5$$

$$100 = 99.6$$

$$100 \approx 99.6$$

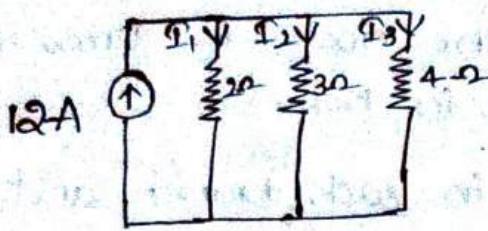Q) By using KCL determine the values of I_1, I_2 , I_3 in the circuit shown in fig.



$$\text{Sol: } I = I_1 + I_2 + I_3$$

$$12 = \frac{V}{2} + \frac{V}{3} + \frac{V}{4}$$

$$12 = \frac{6V + 4V + 3V}{12}$$

$$12 = \frac{13V}{12}$$

$$144 = 13V$$

$$V = \frac{144}{13}$$

$$V = 11.07$$

$$I_1 = \frac{V}{2}$$

$$= \frac{11.07}{2}$$

$$I_1 = 5.5A$$

$$I_2 = \frac{V}{3}$$

$$= \frac{11.07}{3}$$

$$I_2 = 3.67A$$

$$I_3 = \frac{V}{4}$$

$$= \frac{11.07}{4}$$

$$I_3 = 2.77A$$

$$I = I_1 + I_2 + I_3$$

$$12 = 5.5 + 3.67 + 2.77$$

$$12 = 11.8$$

P - short by mistake


$$P = \frac{0.1 - 8V}{1} + 8V + \frac{V - 11}{4}$$

$$0.1 - 8V + 8V + V - 11 = 0$$

Node Analysis :


Node analysis is also known as node voltage analysis (or) Branch current method. It is used to determine voltage b/w the node in terms of branch current. This method used in KCL.

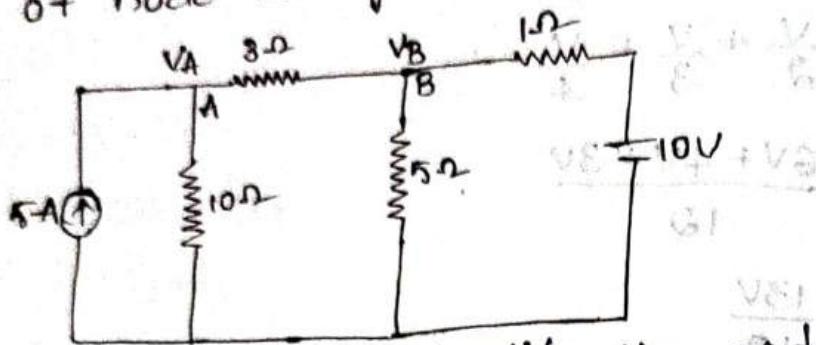* Q) Determine the current in each branch and write the eqⁿ of node voltage in the circuit shown in fig



Sol: In the given circuit identify the nodes A, B & C
Select 'c' node as Reference node.

Assign the variables voltage V_A, V_B

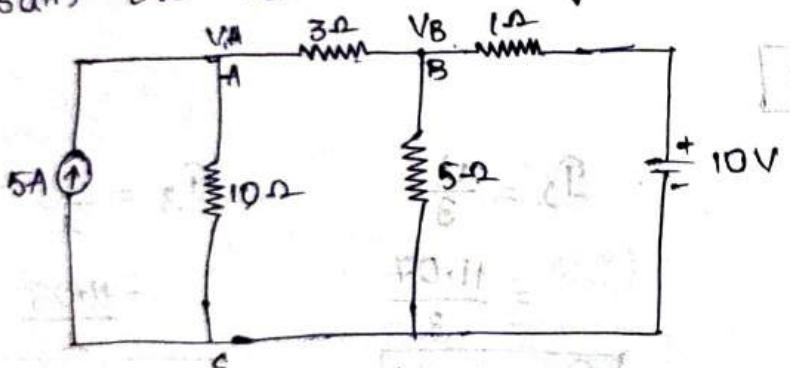

By using KCL node-I

$$5 = \frac{V_A}{10} + \frac{V_A - V_B}{3}$$

$$5 = \frac{3V_A + 10V_B - 10V_B}{30}$$

$$150 = 13V_A - 10V_B \quad \text{--- ①}$$

By using KCL node-II

$$\frac{V_B - V_A}{3} + \frac{V_B}{5} + \frac{V_B - 10}{1} = 0$$

$$\frac{5V_B - 5V_A + 3V_B + 15V_B - 150}{15} = 0$$

$$-5V_A + 23V_B = 150 \quad \text{--- ②}$$

Solving ① & ② eqns and calculate the value of V_A, V_B .

$$⑥ x_1 = 13V_A - 10V_B = 150$$

$$⑦ x_2 = -5V_A + 23V_B = 150$$

$$65V_A - 50V_B = 750$$

$$\underline{-65V_A + 23V_B = 150}$$

$$249V_B = 2700$$

$$V_B = \frac{2700}{249}$$

$$V_B = 10.84 \text{ V}$$

Substitute $V_B = 10.84$ in eq ①

$$13V_A - 10(10.84) = 150$$

$$13V_A - 108.4 = 150$$

$$13V_A = 150 + 108.4$$

$$13V_A = 258.4$$

$$V_A = \frac{258.4}{13}$$

$$V_A = 19.87 \text{ V}$$

$$\text{Current in } 10\Omega = I = \frac{V}{R} = \frac{V_A}{R} = \frac{19.87}{10}$$

$$= 1.987 \text{ V. } \text{ SUPPLY ALONE}$$

$$\text{Current in } 3\Omega = \frac{V_A - V_B}{R} = \frac{19.87 - 10.84}{3} = \frac{9.03}{3}$$

$$= 3.01 \text{ A}$$

$$\text{Current in } 5\Omega = \frac{V_B}{R} = \frac{V_B}{5} = \frac{10.84}{5}$$


$$= 2.168 \text{ A}$$

$$\text{Current in } 1\Omega = \frac{V_B - 10}{1} = \frac{10.84 - 10}{1}$$

$$= 0.84 \text{ A.}$$

$$V_B = 10.84 \text{ V}$$

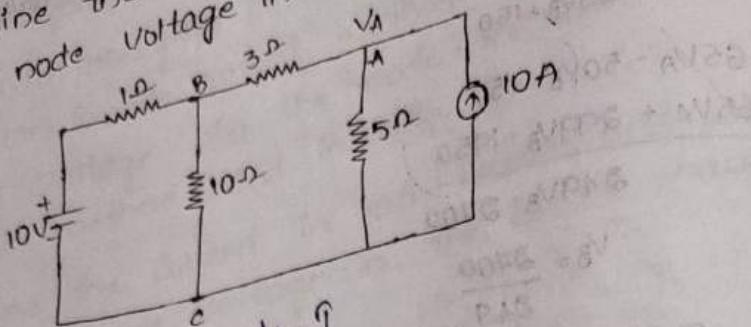Q) Determine the current in each branch shown in fig.



Sol: By using KCL node - I

$$10 = \frac{V_A}{5} + \frac{V_A - V_B}{3}$$

$$10 = \frac{3V_A + 5V_A - 5V_B}{15}$$

$$150 = 8V_A - 5V_B \quad \text{--- (1)}$$

By using KCL node - II

$$\frac{V_B - V_A}{3} + \frac{V_B}{10} + \frac{V_B - 10}{1} = 0$$

$$\frac{10V_B - 10V_A + 3V_B + 30V_B - 300}{300} = 0$$

$$-10V_A + 43V_B - 300 = 0$$

$$-10V_A + 43V_B = 300 \quad \text{--- (2)}$$

solving eqn ① & ② and calculate of values $V_A - V_B$

$$10 \times ① 150 = 8V_A - 5V_B$$

$$8 \times ② 300 = -10V_A + 43V_B$$

$$1500 = 80V_A - 50V_B$$

$$2400 = -80V_A + 344V_B$$

$$3900 = 294V_B$$

$$V_B = \frac{3900}{294}$$

$$V_B = 13.26 \text{ V}$$

$$8V_A - 66 \cdot 3 = 150$$

$$8V_A - 150 + 66 \cdot 3 = 216 \cdot 3$$

$$8V_A = 216 \cdot 3$$

$$V_A = \frac{216 \cdot 3}{8}$$

$$V_A = 27.03$$

current in $5\Omega = \frac{V_A}{5\Omega}$

current in $3\Omega = \frac{V_A}{3\Omega}$

current in $10\Omega = \frac{V_A}{10\Omega}$

current in $1\Omega = \frac{V_A}{1\Omega}$

Energy Sources :

Energy Sources

→ Independent S

→ Dependent Sour

Independent Sour

→ Ideal and Pr


→ Ideal and P

Ideal Voltage
independent

→ The ideal
voltage d

→ When a

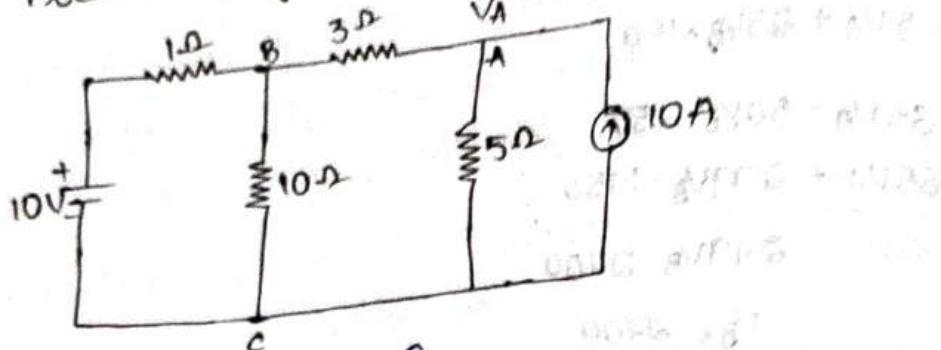Q) Determine the current in each branch and write the eqn node voltage in circuit shown in fig.



Sol: By using KCL node- A

$$10 = \frac{V_A}{5} + \frac{V_A - V_B}{3}$$

$$10 = \frac{3V_A + 5V_A - 5V_B}{15}$$

$$150 = 8V_A - 5V_B \quad \text{--- } ①$$

By using KCL node- B

$$\frac{V_B - V_A}{3} + \frac{V_B}{10} + \frac{V_B - 10}{1} = 0$$

$$\frac{10V_B - 10V_A + 3V_B + 30V_B - 300}{300} = 0$$

$$-10V_A + 43V_B - 300 = 0$$

$$-10V_A + 43V_B = 300 \quad \text{--- } ②$$

solving eqn ① & ② and calculate of values (V_A, V_B)

$$10 \times ① \quad 150 = 8V_A - 5V_B$$

$$8 \times ② \quad 300 = -10V_A + 43V_B$$

$$1500 = 80V_A - 50V_B$$

$$8400 = -80V_A + 344V_B$$

$$3900 = 294V_B$$

$$V_B = \frac{3900}{294}$$

$$V_B = 13.26 \text{ V}$$

Substitute $V_B = 13.26$ in eq 0

$$8V_A - 5(13.26) = 150$$

$$8V_A - 66.3 = 150$$

$$8V_A = 150 + 66.3$$

$$8V_A = 216.3$$

$$V_A = \frac{216.3}{8}$$

$$\boxed{V_A = 27.03V}$$

Current in $5\Omega = \frac{V_A}{5} = \frac{27.03}{5} = 5.406A$

Current in $3\Omega = \frac{V_A - V_B}{3} = \frac{27.03 - 13.26}{3} = \frac{13.77}{3} = 4.59A$

Current in $10\Omega = \frac{V_B}{10} = \frac{13.26}{10} = 1.326A$

Current in $1\Omega = \frac{V_B - 10}{1} = \frac{13.26 - 10}{1} = 3.26A$

Energy Sources :

Energy Sources are classified into two types

→ Independent Source

→ Dependent Source

Independent Sources : Independent Sources are Sub-divided into two types.

i) Ideal and Practical Voltage Source.


ii) Ideal and Practical Current Source.

Ideal Voltage Source : Ideal voltage source, the voltage independent of current source.



→ The ideal voltage source maintain the constant voltage doesn't change.

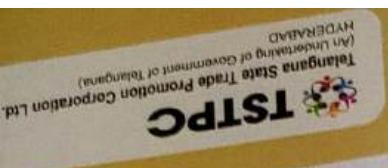→ When a change takes place in electric networks:





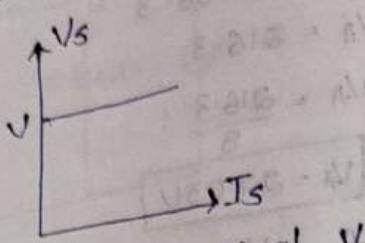
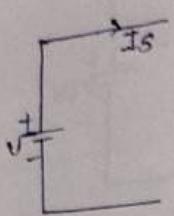
- Ideal voltage source we have zero internal resistance.
- The ideal voltage source are doesn't exist



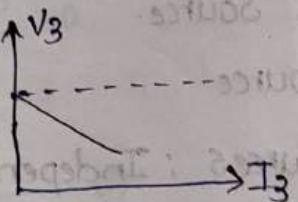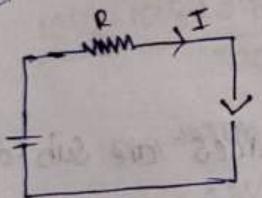i) Practical voltage source: In practical voltage source can be consider as series combination of ideal voltage source and some internal resistance is known as practical voltage source.

→ In practical voltage source depend upon current source.

→ In practical voltage source having some internal resistance due to which decreases the voltage and increases the current.





Ideal current source: Ideal current source, the current source independent of voltage source.


→ Ideal current source maintain the constant current and does not change.

→ When the changes take place in electric networks.

→ Ideal current source doesn't exist.

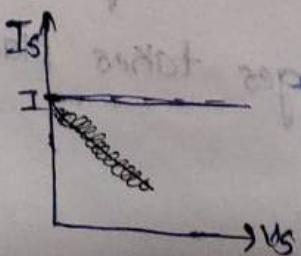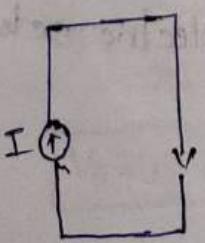

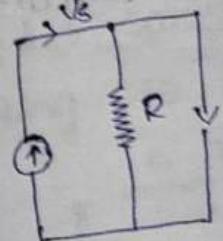- * Practical consider as parallel and same internal current source.
- Practical current upon voltage source.
- Practical current resistance, due increases in



Dependent Source

Dependent

1) Voltage dep

2) Voltage dep

3) Current dep

4) Current dep

Super position

statement:

any linear

the respons



algebraic

acting indi

Note: Rema
circuit. Rem

→ Ideal Voltage Source we have zero internal resistance.

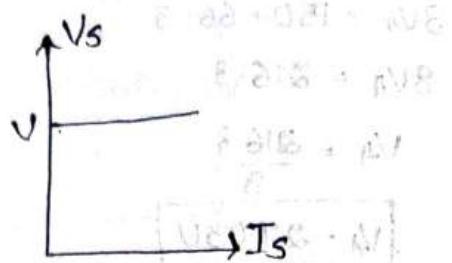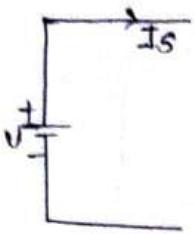→ The ideal voltage source are doesn't exist.





iii) Pro
cone
and curr
→ P
up
→ P
re
ir
D
1
2
3
4

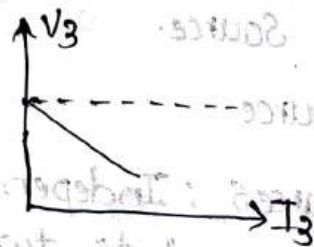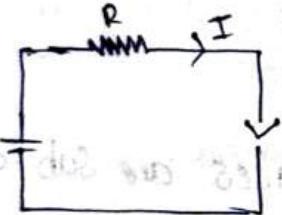i) Practical voltage source: In practical voltage source can be consider as Series combination of ideal voltage source and some internal resistance is known as practical voltage source.

→ In practical voltage source depend upon current source.

→ In practical voltage source having some internal resistance due to which decreases the voltage and increases the current.





Ideal Current Source: Ideal Current Source, the current source independent of voltage source.

→ Ideal current source maintain the constant current and does not change.

→ When the changes take place in electric networks.



→ Ideal current source doesn't exist.

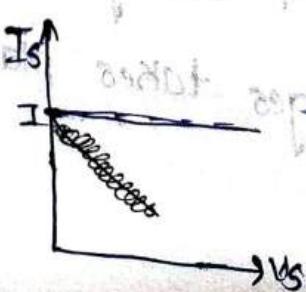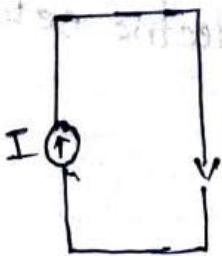

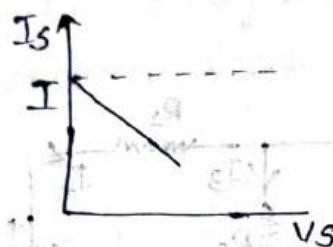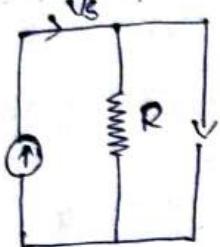iii) Practical Current Source: Practical Current Source can be considered as parallel combination of ideal current source and same internal resistance is known as practical current source.

→ Practical current source the current source depend upon voltage source.

→ Practical current source having the same internal resistance, due to which decreases the current and increases in voltage.



Dependent Source:

Dependent sources classified into four types.

- 1) Voltage dependent voltage source.
- 2) Voltage dependent current source.
- 3) Current dependent voltage source.
- 4) Current dependent current source.


Super position theorem:

Statement: Super position theorem states that in any linear elements containing two (or) more sources, the response of any element is equal to the algebraic sum of the response caused by source are acting individually.


Note: Removal of voltage source means short circuit. Removal of current means open circuit.

& dependent power source will also not affect the result of position

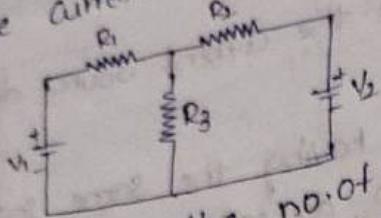
Explanation / verification of Super position theorem:
In the given circuit shown in figure
find the current flowing through various branches.



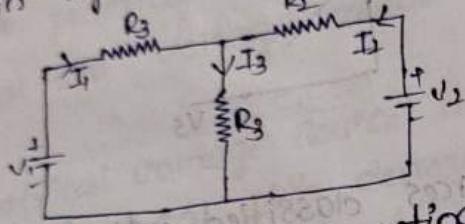Step 1: Identify the no. of branches in the circuit and mark the current direction in each branch.
Let consider I_1 , I_2 & I_3 in the direction circuit is shown in fig.



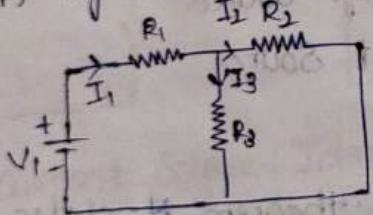Step 2: Let consider V_1 is acting and V_2 is short-circuited according to Super position theorem as shown in fig.



In the above circuit the total resistance R_T is given

$$R_T = \frac{R_2 \times R_3}{R_2 + R_3} + R_1$$

Total current flowing through the circuit is

given


$$I_T = \frac{V_1}{R_T}$$

The current flowing through R_2

According to Current division Rule.

Total current flowing
 $I_2' = I_T \times \frac{R_3}{R_2 + R_3}$
the current flowing
 $I_3' = I_T \times \frac{R_2}{R_2 + R_3}$
By using KCL $I_1' = I_3'$

Step 3: Let consider
According to Super

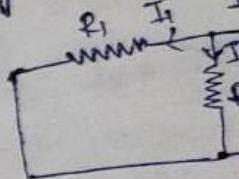

In the above
given by

$$R_{T2} = \frac{R_1 \times R_2}{R_1 + R_2}$$

Total current
by

$$I_2'' = \frac{V_2}{R_{T2}}$$

The current


$$I_1'' =$$

The current


$$I_3'' =$$

By using

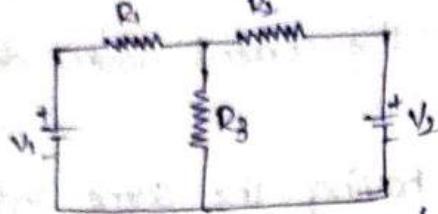
Exploration / verification of super position theorem:
In the given circuit shown in figure
find the current flowing through various branches.



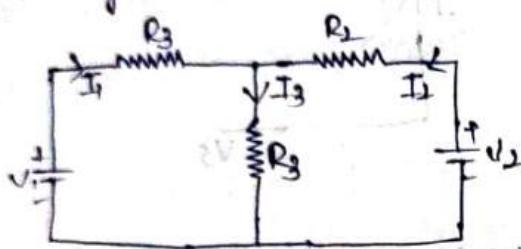Step 1: Identify the no. of branches in the circuit and mark the current direction in each branch.
Let consider I_1 , I_2 & I_3 in the direction circuit is shown in fig.



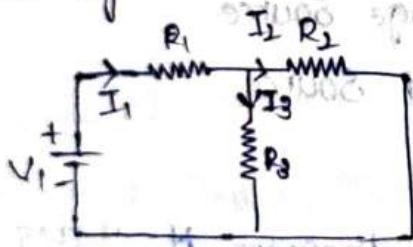Step 2: Let consider V_1 is acting and V_2 is short-circuited according to Super position theorem as shown in fig.



In the above circuit the total resistance R_T is given

$$R_T = \frac{R_2 \times R_3}{R_2 + R_3} + R_1$$

Total current flowing through the circuit is given

$$I_T = \frac{V_1}{R_T}$$

The current flowing through R_2 According to Current division Rule.

Total Current $\times \frac{\text{opposite Resistance}}{\text{opp.resi} + \text{sum of the resis}}$

$$I_2' = I_1' \times \frac{R_3}{R_2 + R_3}$$


the current flowing through R_3

$$I_3' = I_1' \times \frac{R_2}{R_2 + R_3}$$

By using KCL, $I_1' = I_2' + I_3'$

$$I_3' = I_1' - I_2'$$

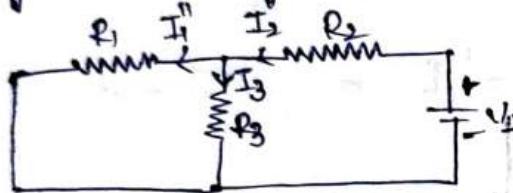Step 3: Let consider V_2 is acting and V_1 is short circuit
According to Super position theorem as shown in fig



In the above circuit the total resistance R_{T2} is given by

$$R_{T2} = \frac{R_1 \times R_2}{R_1 + R_2} + R_3$$

Total current flowing through the circuit is given by

$$I_2'' = \frac{V_2}{R_{T2}}$$

The current flowing through R_2

$$I_2'' = I_2'' \times \frac{R_2}{R_2 + R_3}$$

The current flowing through R_3

$$I_3'' = I_2'' \times \frac{R_1}{R_1 + R_2}$$

By using KCL $I_2'' = I_1'' + I_3''$

$$I_3'' = I_2'' - I_1''$$

$$0.08 + 0.08 = 0.16$$

$$0.08 - 0.08 = 0.00$$

Step 4:


The resultant direction of current in various branches is given as the resultant direction of current

$$I_1 = I_1' - I_1'' \text{ (or) } I_1 = I_1'' - I_1' \quad [\text{opposite direction in both cases}]$$

$$\text{the resultant direction of current } I_2 = I_2' - I_2'' \text{ (or) } I_2 = I_2'' - I_2' \quad [\text{opposite direction in both cases}]$$


$$\text{The resultant direction of current } I_3 = I_3' + I_3'' \quad [\text{same direction in both cases}].$$

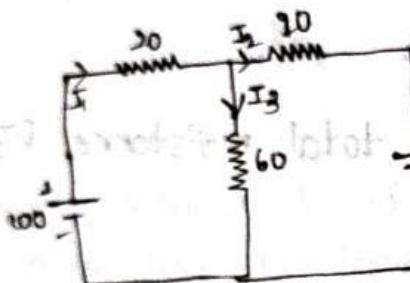* In the circuit shown in fig find the current flow through various branches



Sol: Let us consider 100V is acting and 70V is in short circuit.

According to Super position theorem:

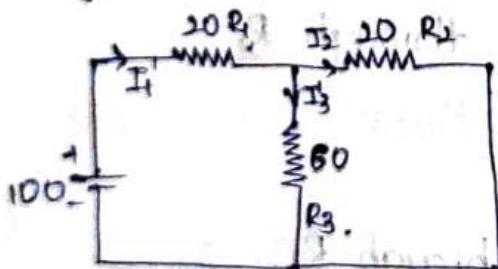

In the above circuit total resistance R_{T1} is 20 & 60 are in |||||

$$R_{T1} = \frac{20 \times 60}{20 + 60} \Rightarrow \frac{1200}{80}$$

$$R_{T1} = 15\Omega$$

15Ω & 20Ω are in Series

$$R_{T1} = 15 + 20$$

$$\boxed{R_{T1} = 35\Omega}$$

Total current flowing through the circuit

$$I'_1 = \frac{V_1}{R_1} \Rightarrow I'_1 = \frac{100}{35}$$

$$= 2.85$$

$$I'_1 = 2.85A$$

According to current division rule
current flowing through $R_2 = 20\Omega$

$$I'_2 = I'_1 \times \frac{R_2}{R_2 + R_3}$$

$$I'_2 = 2.85 \times \frac{60}{60+20}$$

$$I'_2 = \frac{2.85}{100} \times \frac{60}{80}$$

$$I'_2 = \frac{855}{4 \times 100} \Rightarrow I'_2 = \frac{213.75}{100}$$

$$I'_2 = 2.1375A$$

$$\boxed{I'_2 = 2.13A}$$

Current flowing through $R_3 = 60\Omega$

$$I'_3 = I'_1 \times \frac{R_3}{R_2 + R_3}$$

$$I'_3 = 2.85 \times \frac{20}{20+60}$$

$$I'_3 = \frac{2.85}{100} \times \frac{20}{80} \Rightarrow I'_3 = \frac{2.85}{4 \times 100}$$

$$I'_3 = \frac{71.25}{100} \Rightarrow I'_3 = 0.7125$$

$$\boxed{I'_3 = 0.71A}$$


By using KCL $I'_1 = I'_2 + I'_3$

$$2.85 = 2.13 + 0.71$$

$$2.85 \approx 2.84$$

$$S_3 = S$$

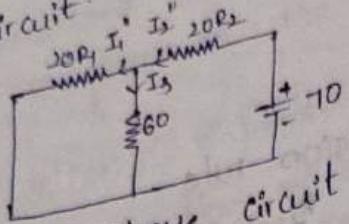Let consider 70V is acting and 100V is in short circuit.



In the above circuit total resistance R_{T1} is $20 + 60$ are in parallel

$$R_{\text{eq}} = \frac{20 \times 60}{20 + 60} = \frac{1200}{80} = 15 \Omega$$

$15 \Omega + 20 \Omega$ are in series

$$R_{T2} = 15 + 20 = 35 \Omega$$

Total Current flowing through the circuit is

$$I_2'' = \frac{V_2}{R_{T2}} \Rightarrow I_2'' = \frac{70}{35}$$

$$I_2'' = 2A$$

According to current division rule

Current flowing through $R_1 = 20 \Omega$

$$I_1'' = I_2'' \times \frac{R_1}{R_1 + R_2}$$

$$I_1'' = 2 \times \frac{60}{80} \Rightarrow I_1'' = 2 \times \frac{60}{80} \Rightarrow I_1'' = 3/2$$

$$I_1'' = 1.5A$$

current flowing through $R_3 = 60 \Omega$

$$I_3'' = I_2'' \times \frac{R_3}{R_1 + R_3}$$

$$I_3'' = 2 \times \frac{60}{80} \Rightarrow I_3'' = 2 \times \frac{60}{80} \Rightarrow I_3'' = 1/2$$

$$I_3'' = 0.5A$$

By using KCL $I_2'' = I_1'' + I_3''$


$$2 = 1.5 + 0.5$$

$$2 = 2$$

branches is given
in $I_1 = I_1' - I_1''$
 $\Rightarrow I_1 = 2.85$
 $\Rightarrow I_1 = 1.35$
resultant direction

resultant direction

Q) In the circuit flowing through

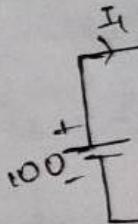

Sol: Let us
short-circuited


According

In the

20 & 160

Req =

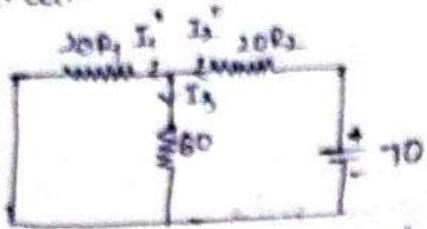→ Let consider 90V is acting and 100V is in short circuit.



In the above circuit total resistance R_T is 20 & 60 are in parallel

$$R_{\text{eq}} = \frac{20 \times 60}{20 + 60} = \frac{1200}{80} = 15\Omega$$

15Ω & 20Ω are in series

$$R_T = 15 + 20 = 35\Omega$$

Total current flowing through the circuit is

$$I_2'' = \frac{V_2}{R_T} \Rightarrow I_2' = \frac{70}{35}$$

$$\boxed{I_2'' = 2A}$$

According to current division rule

Current flowing through $R_1 = 20\Omega$

$$I_1'' = I_2'' \times \frac{R_1}{R_1 + R_2}$$

$$I_1' = 2 \times \frac{60}{80} \Rightarrow I_1'' = 2 \times \frac{60}{80} \Rightarrow I_1'' = 3/2$$

$$\boxed{I_1' = 1.5A}$$

current flowing through $R_3 = 60\Omega$

$$I_3'' = I_2'' \times \frac{R_3}{R_1 + R_3}$$

$$I_3' = 2 \times \frac{20}{80} \Rightarrow I_3'' = 2 \times \frac{20}{80} \Rightarrow I_3'' = 1/2$$

$$\boxed{I_3'' = 0.5A}$$

By using KCL $I_2' = I_1' + I_3''$

$$2 = 1.5 + 0.5$$

$$2 = 2$$

The resultant direction of current in various branches is given by the resultant direction of current in $I_1 = I_1' - I_1''$

$$\Rightarrow I_1 = 2.85 - 1.5$$

$$\Rightarrow I_1 = 1.35 \text{ A}$$

resultant direction of current in $I_2 = I_2' - I_2''$

$$\Rightarrow I_2 = 2.13 - 2.0$$

$$\Rightarrow I_2 = 0.13 \text{ A}$$


resultant direction of current $I_3 = I_3' + I_3''$

$$I_3 = 0.71 + 0.5$$

$$\boxed{I_3 = 1.21 \text{ A}}$$


~~Ans. 1.21 A~~

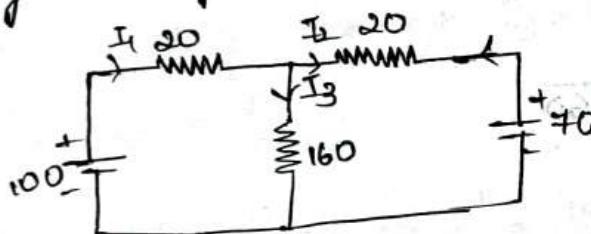Q) In the circuit shown in fig. find the currents flowing through various branches.



Sol: Let us consider 100V is acting and 70V is in short-circuit

According to Super position theorem

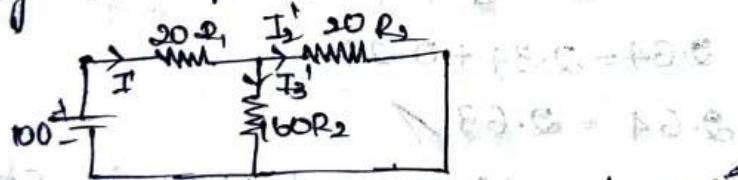

In the above circuit total resistance R_{T1} is $20 + 160$ are in Net.

$$R_{\text{eq}} = \frac{20 \times 160}{20 + 160} = \frac{3200}{180}$$

$$R_{\text{eq}} = 17.77 \Omega$$

$17.77 + 20\Omega$ are in Series.

$$R_{T1} = 17.77 + 20$$

$$\boxed{R_{T1} = 37.77 \Omega}$$

Total current flowing through the circuit

$$I_1' = \frac{V_1}{R_{T1}} \Rightarrow I_1' = \frac{100}{37.77} \Rightarrow I_1' = 2.64\text{A}$$

According to current division rule

Current flowing through $R_2 = 20\Omega$

$$\rightarrow I_2' = I_1' \times \frac{R_2}{R_2 + R_3}$$

$$\rightarrow I_2' = 2.64 \times \frac{20}{20+160}$$

$$\rightarrow I_2' = \frac{264}{100} \times \frac{160}{180}$$

$$I_2' = 2.34\text{A}$$

Current flowing through $R_3 = 160\Omega$

$$\rightarrow I_3' = I_1' \times \frac{R_3}{R_2 + R_3}$$

$$\rightarrow I_3' = 2.64 \times \frac{160}{20+160}$$

$$\rightarrow I_3' = \frac{264}{100} \times \frac{20}{180}$$


$$I_3' = 0.29\text{A}$$

By using KCL $I_1' = I_2' + I_3'$

$$2.64 = 2.34 + 0.29$$

$$2.64 = 2.63$$

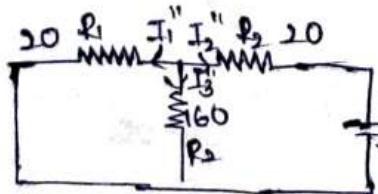\rightarrow Let consider 70V is acting and 100V is short circuit



In the above circuit total resistance R_T is 20 & 160 are in |||

$$R_{T1} = \frac{20 \times 160}{20 + 160} = \frac{3200}{180} = 17.78$$

17. 77 & 20 are in series

$$R_{T_2} = 17 + 77 + 20$$

$$R_{T_2} = 37 + 77$$

Total current flowing through the circuit is

$$I_2'' = \frac{V_2}{R_{T_2}} = \frac{40}{37 + 77}$$

$$I_2'' = 1.85 \text{ A}$$

According to current division rule
current flowing through $R_1 = 20 \Omega$

$$\Rightarrow I_1'' = I_2'' \times \frac{R_1}{R_2 + R_1}$$

$$\Rightarrow I_1'' = 1.85 \times \frac{160}{160 + 20} \Rightarrow I_1'' = \frac{1.85}{100} \times \frac{160}{180}$$

$$\Rightarrow I_1'' = 1.64 \text{ A}$$

Current flowing through $R_3 = 160 \Omega$

$$\Rightarrow I_3'' = I_2'' \times \frac{R_3}{R_1 + R_3}$$

$$\Rightarrow I_3'' = 1.85 \times \frac{20}{20 + 160} \Rightarrow I_3'' = \frac{1.85}{100} \times \frac{20}{180}$$

$$I_3'' = 0.205 \text{ A}$$

By using KCL $\Rightarrow I_1'' = I_1' + I_3''$

$$\Rightarrow 1.85 = 1.64 + 0.20$$

$$\Rightarrow 1.85 = 1.84$$

The resultant direction of current in $I_1 = I_1' - I_1''$

$$\Rightarrow I_1 = 2.64 - 1.64$$

$$\Rightarrow I_1 = 1 \text{ A}$$

The resultant direction of current in $I_2 = I_2' - I_2''$


$$\Rightarrow I_2 = 2.84 - 1.85$$

$$I_2 = 0.49 \text{ A}$$


The resultant direction of current in $I_3 = I_3' + I_3''$

$$\Rightarrow I_3 = 0.29 + 0.205 \Rightarrow 0.495$$

$$I_3 = 0.495 \text{ A}$$

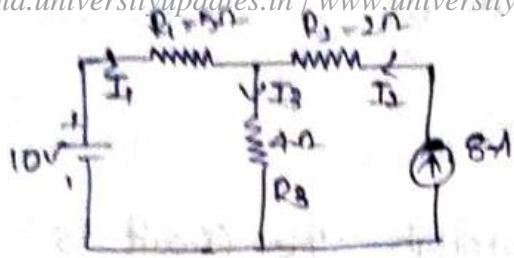

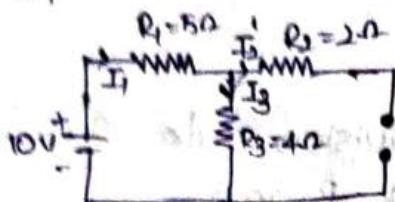Step 2: Let consider V is acting and Current Source is open.



$$R_{T1} = 5 + 4$$

$$= 9\Omega$$

$$\text{Total Current } I_1' = \frac{V}{R_{T1}} = \frac{10}{9} = 1.11\text{ A}$$

$$I_2' = 0$$


$I_1' = I_3'$ these are in series

$$\text{By using KCL } I_1' = I_2' + I_3' \Rightarrow 1.11 = 0 + 1.11$$

$$1.11 = 1.11$$

Step 3:

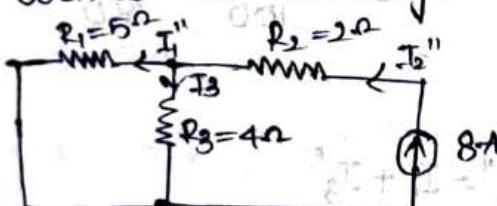Current source is acting, voltage source is short



The current flowing through R_1 is $I_1'' = 8\text{ A}$

$$I_1'' = I_2'' \times \frac{R_3}{R_3 + R_1} \Rightarrow I_1'' = 8 \times \frac{4}{4+5}$$

$$\Rightarrow I_1'' = \frac{32}{9} \Rightarrow I_1'' = 3.56\text{ A}$$

$$I_3'' \Rightarrow I_2'' \times \frac{R_1}{R_1 + R_3} \Rightarrow I_3'' = 8 \times \frac{5}{9+5} \Rightarrow I_3'' = \frac{40}{9}$$

$$\Rightarrow I_3'' = 4.44\text{ A}$$

$$\text{By using } I_1'' = I_3'' + I_1''$$

$$8 = 4.44 + 3.56$$

$$8 = 7.99 \approx 8$$

the resultant direction of current $I_1 = I_1' + I_1''$

$$\Rightarrow I_1 = 3.5 - 1.1$$

$$\Rightarrow I_1 = 2.4 \text{ A}$$

the resultant direction of current $I_2 = I_2' - I_2''$

$$\Rightarrow I_2 = 8 - 0$$


$$I_2 = 8 \text{ A}$$

the resultant direction of current $I_3 = I_3' + I_3''$

$$\Rightarrow I_3 = 4.4 + 1.1$$


$$\Rightarrow I_3 = 5.5 \text{ A}$$

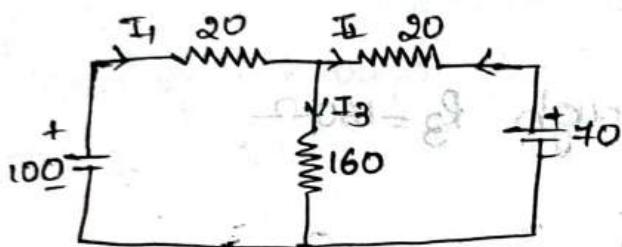(a) In the circuit shown in fig. find the Current flowing through various branches.



Sol: let us consider 100V is acting and 70V is in short circuit.

According to Super position theorem

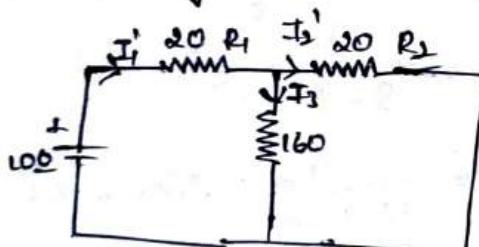

In the above circuit total resistance R_{T1} is $20 + 160$ are in parallel

$$R_{\text{eq}} = \frac{20 \times 160}{20 + 160} = \frac{3200}{180} = 17.77 \Omega$$

$$R_{\text{eq}} = 17.77 \Omega$$

17.77 & 20 ohms are in series

$$R_{T1} = 17.77 + 20$$

$$R_{T1} = 37.77 \Omega$$

Total current flowing through the circuit

$$I_1' = \frac{V_1}{R_1} \Rightarrow I_1' = \frac{100}{37.77}$$

$$I_1' = 2.64 \text{ A}$$

According to current division rule
current flowing through $R_2 = 20 \Omega$

$$I_2' = I_1' \times \frac{R_2}{R_2 + R_3}$$

$$\Rightarrow I_2' = 2.64 \times \frac{160}{160 + 20}$$

$$\Rightarrow I_2' = \frac{264}{100} \times \frac{160}{180}$$

$$\Rightarrow I_2' = 2.34 \text{ A}$$

Current flowing through $R_3 = 160 \Omega$

$$\Rightarrow I_3' = I_1' \times \frac{R_3}{R_2 + R_3}$$

$$\Rightarrow I_3' = 2.64 \times \frac{20}{20 + 160}$$

$$\Rightarrow I_3' = \frac{264}{100} \times \frac{20}{180}$$


$$I_3' = 0.29 \text{ A}$$

By using KCL $I_1' = I_2' + I_3'$

$$2.64 = 2.34 + 0.29$$

$$2.64 = 2.63$$

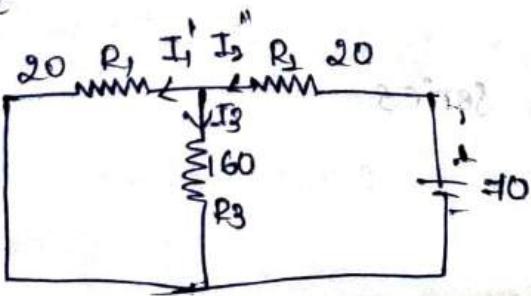→ Let consider 70V is acting and 100V is short-circuit



In the above circuit total resistance R_T is

20 & 160 are in parallel

$$R_{eq} = \frac{20 \times 160}{20 + 160} = \frac{3200}{180} = 17.77$$

17.77 & 20 are in series

$$R_T = 17.77 + 20$$

$$R_T = 37.77$$

Total current flowing through the circuit is

$$I_2'' = \frac{V_2}{R_T} = \frac{40}{37.77}$$

$$I_2'' = 1.085 A$$

According to Current division rule:

current flowing through $R_1 = 20 \Omega$

$$\Rightarrow I_1' = I_2'' \times \frac{R_1}{R_1 + R_3}$$

$$\Rightarrow I_1' = 1.085 \times \frac{160}{160 + 20} \Rightarrow I_1' = \frac{185}{100} \times \frac{160}{180}$$

$$I_1' = 1.64 A$$

Current flowing through $R_3 = 160 \Omega$

$$I_3'' = I_2'' \times \frac{R_3}{R_1 + R_3}$$

$$I_3'' = 1.085 \times \frac{20}{20 + 160} \Rightarrow I_3'' = \frac{185}{100} \times \frac{20}{180}$$

$$I_3'' = 0.205 A$$

By using KCL $\Rightarrow I_2'' = I_1' + I_3''$

$$1.085 = 1.64 + 0.20$$

$$1.085 = 1.84$$

The resultant direction of current is $I_1 = I_1' - I_3''$

$$1.085 - 0.205 \rightarrow I_1 = 1.64 - 0.20$$


$$I_1 = 1 A$$

The resultant direction of current in $I_3 = I_3' - I_3''$
 $\Rightarrow I_3' = 0.34 - 1.85$
 $I_3 = 0.499 A$

The resultant direction of current in $I_3 = I_3' + I_3''$
 $I_3 = 0.39 + 0.205$
 $I_3 = 0.495 A$

Home work problem

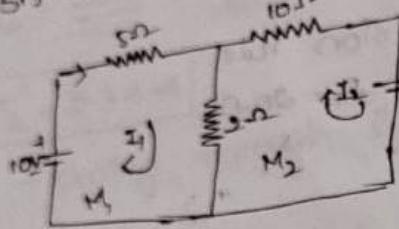(Q) Determine the current and write the equation of mesh current in a circuit as shown in fig




Sol: In the given circuit a closed path so the mesh analysis is applicable

In the given circuit consisting of two closed loops (M_1 & M_2) and assign a variable of current

In the circuit I_1 & I_2

Applying KVL Loop - I

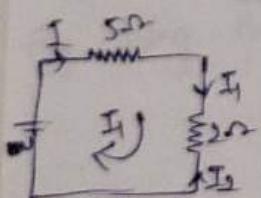


$$\Rightarrow 10 = 5I_1 + 2(I_1 - I_2)$$

$$10 = 5I_1 + 2I_1 - 2I_2$$

$$10 = 7I_1 - 2I_2 \quad \text{--- (1)}$$

Applying KVL loop - II

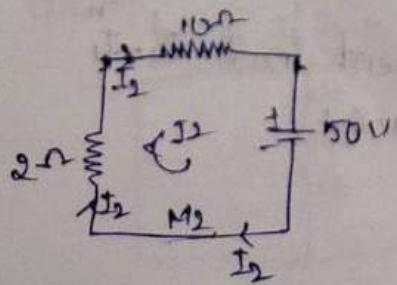

$$\Rightarrow 50 = 2(I_2 - I_1) + 10I_2$$

$$-50 = 2I_2 - 2I_1 + 10I_2$$


$$-50 = -2I_1 + 12I_2 \quad \text{--- (2)}$$

$$6 \times 1 \rightarrow 10 = 2I_1 - 2I_2$$

$$2 \rightarrow -50 = -2I_1 + 12I_2$$

Substitute $I_1 = 0.25$
 $10 = 2(0.25) -$
 $10 - 1.25 =$

(Q) Determine the
- Super position

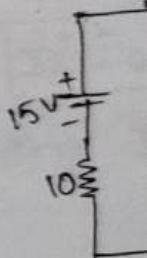

Sol: Step 1 : I
and m...

The total

By U

The resultant direction of current in $I_3 = I_3' - I_3''$

$$\rightarrow I_3' = 0.34 - 1.85$$

$$I_3 = 0.49 A$$


The resultant direction of current in $I_3 = I_3' + I_3''$

$$I_3 = 0.29 + 0.205$$

$$I_3 = 0.495 A$$

Homework Problem

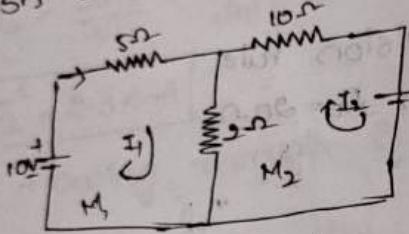(Q) Determine the current and write the equation of mesh current in a circuit as shown in fig




Sol: In the given circuit a closed path so the mesh analysis is applicable

In the given circuit consisting of two closed loops (M_1 & M_2) and assign a variable of current

In the circuit I_1 & I_2

Applying KVL Loop - I

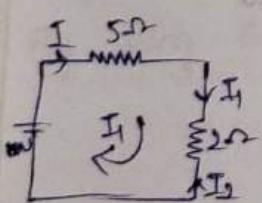


$$\Rightarrow 10 = 5I_1 + 2(I_1 - I_2)$$

$$10 = 5I_1 + 3I_1 - 2I_2$$

$$10 = 7I_1 - 2I_2 \quad \text{--- (1)}$$

Applying KVL loop - II

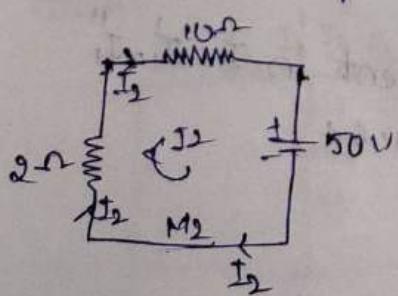

$$\Rightarrow -50 = 2(I_2 - I_1) + 10I_2$$

$$-50 = 2I_2 - 2I_1 + 10I_2$$

$$-50 = -2I_1 + 12I_2 \quad \text{--- (2)}$$

$$6 \times 1 \rightarrow 10 = 7I_1 - 2I_2$$

$$2 \rightarrow -50 = -2I_1 + 12I_2$$

Substitute $I_1 =$

$$10 = 7(0.3)$$

$$10 = 1.75$$

(Q) Determine
- Super position

Sol: Step 1 :
and m

[The tot

The resultant direction of current in $I_3 = I_3' - I_3''$

$$\Rightarrow I_3' = 9.34 - 1.85$$

$$I_3 = 0.49 \text{ A}$$


The resultant direction of current in $I_3 = I_3' + I_3''$

$$I_3 = 0.29 + 0.205$$

$$I_3 = 0.495 \text{ A}$$

Home work problem

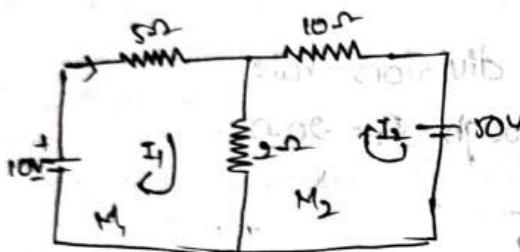(Q) * Determine the current and write the equation of mesh current in a circuit as shown in fig




Sol: In the given circuit a closed path so the mesh analysis is applicable

In the given circuit consisting of two closed loops (M_1 & M_2) and assign a variable of current

In the circuit I_1 & I_2

Applying KVL Loop - I

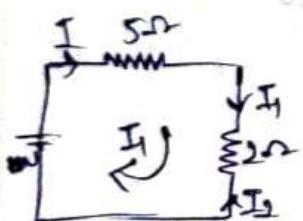


$$\Rightarrow 10 = 5I_1 + 2(I_1 - I_2)$$

$$10 = 5I_1 + 3I_1 - 2I_2$$

$$10 = 7I_1 - 2I_2 \quad \text{--- (1)}$$

Applying KVL loop - II

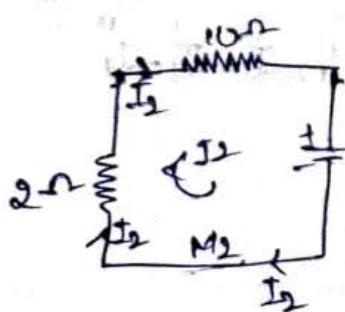

$$\Rightarrow 50 = 2(I_2 - I_1) + 10I_2$$

$$50 = 2I_2 - 2I_1 + 10I_2$$

$$50 = -2I_1 + 12I_2 \quad \text{--- (2)}$$

By using ① & ②

$$6 \times 1 \rightarrow 10 = 7I_1 - 2I_2 \Rightarrow 60 = 42I_1 - 12I_2$$

$$2 \rightarrow -50 = -2I_1 + 12I_2 \Rightarrow \frac{-50}{10} = -2I_1 + 12I_2$$

$$I_1 = 1/4$$

$$I_1 = 0.25A$$

Substitute $I_1 = 0.25A$ in eq ①


$$10 = 7(0.25) - 2I_2 \Rightarrow 10 = 1.75 - 2I_2$$

$$10 - 1.75 = -2I_2 \Rightarrow -2I_2 = 8.25$$


$$I_2 = \frac{-8.25}{2}$$

$$I_2 = -4.125A$$

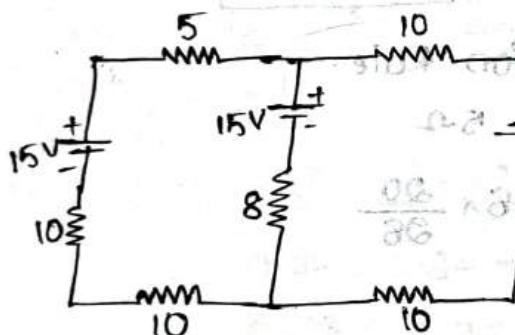(Q) Determine the current in each branch by using super position theorem in the circuit shown in fig.



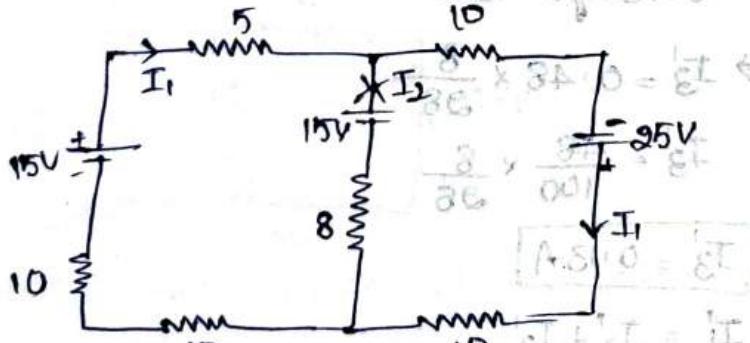Sol: Step 1: Identify the no. of branches in the circuit and mark the direction of current in the circuit.




The total resistance $R_T = R_1 + R_2$

$$R_T = 20 + 15$$

$$R_T = 35$$

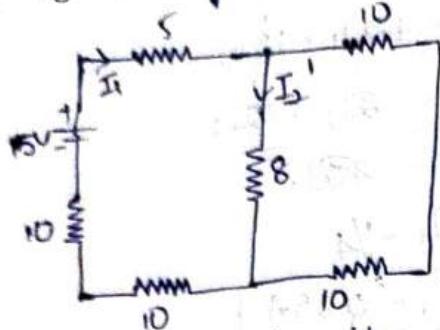According
Let V_1 is acting V_2 & V_3 are short circuit



Total resistance of the circuit R_{T1}

$$R_{T1} = 10 + 10$$

$$= 20$$

$$= \frac{20 \times 8}{20 + 8} = \frac{160}{28}$$

$$= 5.71$$

$$R_{T1} = 5 + 5.71 + 10 + 10 \rightarrow 10.71 + 10 + 10$$

$$R_{T1} = 30.71$$

Total current flowing through the circuit

$$I_1' = \frac{V_1}{R_{T1}} \Rightarrow I_1' = \frac{15}{30.71} \Rightarrow I_1' = 0.48A$$

According to Current division Rule.

Current flowing through 5Ω

$$I_2' = I_1' \times \frac{20}{20+8} \Rightarrow I_2' = 0.48 \times \frac{20}{28}$$

$$I_2' = \frac{48}{100} \times \frac{20}{28}$$

$$I_2' = 0.34A$$

Current flowing through 10Ω

$$I_3' = I_1' \times \frac{8}{8+20} \Rightarrow I_3' = 0.48 \times \frac{8}{28}$$

$$I_3' = \frac{48}{100} \times \frac{8}{28}$$

$$I_3' = 0.13A$$

By using KCL: $I_1' = I_2' + I_3'$

$$0.48 = 0.34 + 0.13$$

$$0.48 \approx 0.48$$

25 & 20 are in parallel

$$\frac{1}{25} + \frac{1}{20} \Rightarrow \frac{20+25}{20 \times 25} \Rightarrow \frac{45}{500} \Rightarrow \frac{1}{R_{T2}} = \frac{45}{500}$$

$$RT_2 = \frac{500}{45}$$

$$RT_2 = 19.11 \Omega$$

Total current flowing through the circuit

$$I_2'' = \frac{V_2}{RT_2} \Rightarrow I_2'' = \frac{15}{19.11}$$

$$I_2'' = 0.78 A$$

current flowing through the 5Ω

$$I_1' = I_2'' \times \frac{20}{20+25} \Rightarrow I_1' = I_2'' \times \frac{20}{45}$$

$$I_1' = 0.78 \times \frac{20}{45} \Rightarrow I_1' = \frac{78}{100} \times$$

$$I_1' = 0.34 A$$

current flowing through 10Ω

$$I_3'' = I_2'' \times \frac{25}{25+20} \Rightarrow I_3'' = 0.78 \times \frac{25}{45}$$

$$I_3'' = \frac{78}{100} \times \frac{25}{45} \Rightarrow I_3'' = \frac{78 \times 5}{900}$$

$$I_3'' = 0.43 A$$


By using KCL: $I_2'' = I_1' + I_3''$

$$0.78 = 0.34 + 0.43$$

$$0.78 \approx 0.78$$

Step 4: $E + 10 + 10 - 25 = 0$ (To find total load voltage)

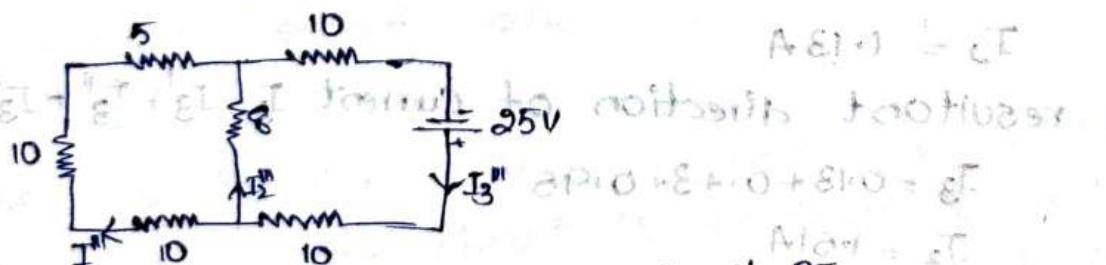V_3 is acting V_1 & V_2 are short circuit.



Total resistance of the circuit RT_3

$$10 + 10 + 5 = 25 \text{ (Series)}$$

$$\frac{25 \times 8}{25+8} = \frac{200}{33} = 6.06 \text{ (parallel)}$$

$$6.06 + 20 = 26.06 \text{ (Series)}$$

$$RT_3 = 26.06$$

+ Total Current flowing through the circuit
 Not for Sale

$$I_3''' = \frac{V_3}{R_{T_3}} \Rightarrow I_3''' =$$

$$I_3''' = \frac{25}{26.06} \Rightarrow I_3''' = 0.95 A$$

Current flowing through 10Ω

$$I_1''' = I_3''' \times \frac{8}{8+25} \Rightarrow I_1''' = 0.95 \times \frac{8}{33}$$

$$I_1''' = \frac{95}{100} \times \frac{8}{33} \Rightarrow I_1''' = 0.23 A$$

Current flowing through 8Ω

$$I_2''' = I_3''' \times \frac{25}{25+8} \Rightarrow I_2''' = 0.95 \times \frac{25}{33}$$

$$I_2''' = \frac{95}{100} \times \frac{25}{33} \Rightarrow I_2''' = 0.71 A$$

By using KCL: $I_3''' = I_1''' + I_2'''$

$$0.95 = 0.23 + 0.71$$

$$0.95 \approx 0.94$$

Step 5: the resultant direction of current is given by

The resultant direction of current $I_1 = I_1' - I_1'' + I_1'''$

$$\Rightarrow I_1 = 0.48 - 0.34 + 0.23$$

$$\Rightarrow I_1 = 0.37 A$$

The resultant direction of current $I_2 = -I_2' + I_2'' + I_2'''$

$$\Rightarrow I_2 = -0.36 + 0.78 + 0.71$$


$$I_2 = 1.13 A$$

The resultant direction of current $I_3 = I_3' + I_3'' + I_3'''$


$$I_3 = 0.13 + 0.43 + 0.95$$

$$I_3 = 1.51 A$$

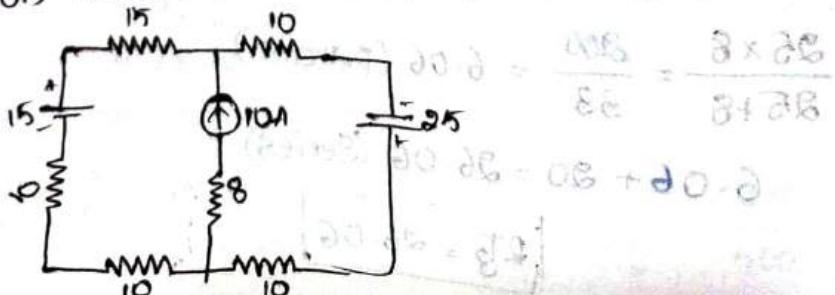
Q) Determine the current in each branch by using Super position theorem in the circuit shown in fig.



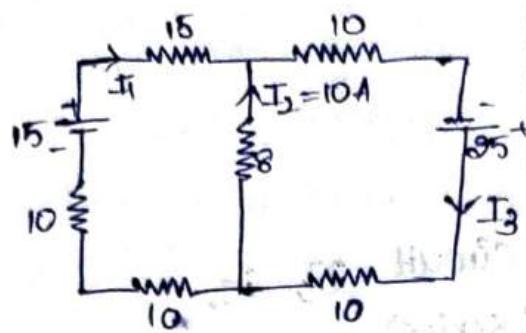Sol: Step 1: Identify the no. of branches in the circuit and mark the direction of current in the circuit.



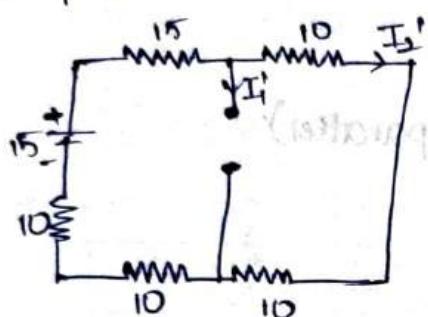Step 2: Let V_1 is acting & I is open, $\frac{V_1}{R}$ is short according to Super position theorem.



Total resistance of the circuit

$$RT_1 = 15 + 10 + 10 + 10 + 10$$

$$RT_1 = 55\Omega$$

Total current in the circuit

$$I_1' = \frac{V_1}{RT_1} \Rightarrow I_1' = \frac{15}{55}$$

$$I_1' = 0.27 A$$

Current flowing through 10Ω

$$I_3' = I_1'$$

\therefore Because flowing through 10Ω

$$I_3' = I_1' \times$$

\therefore Because as the 8Ω resistance current does not pass.

Hence the $[I_2' = 0A]$, The circuit is in Series connection so the current I_1' flows through as the resistance.



$$\therefore [I_3' = I_1' = 0.27 A]$$

By using KCL: $I_1' = I_2' + I_3'$

$$0.27 = 0 + 0.27$$

$$0.27 = 0.27$$

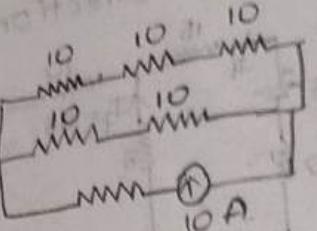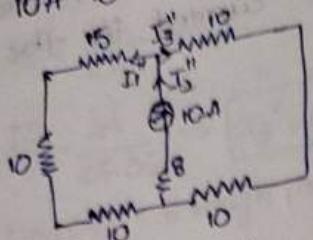Step 3: Let $10A$ is acting & V_3 is short circuit




Total resistance of the circuit R_T is

$$R_T = 10 + 10 = 20 \text{ (series)}$$

$$10 + 10 + 15 = 35 \text{ (series)}$$

$$(R_T = \frac{20 \times 35}{20 + 35} \rightarrow R_T = \frac{300}{55})$$

$$R_T = 12.72\Omega$$

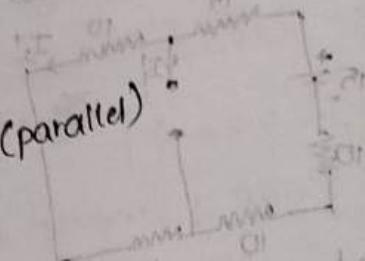

$$R_T = 12.72 + 8 \\ = 20.72 \text{ (series)}$$

$$\therefore R_T = 20.72\Omega$$

Total current flowing through the circuit

$$I_2'' = 10A \text{ (given)}$$

Current flowing through 15Ω

$$I_1'' = I_2'' \times \frac{20}{20 + 35} \Rightarrow I_1'' = 10 \times \frac{20}{55}$$

$$I_1'' = \frac{200}{55} \Rightarrow I_1'' = 3.63A$$

current flowing through 10Ω

$$I_3'' = I_2'' \times \frac{35}{35 + 20} \Rightarrow I_3'' = 10 \times \frac{35}{55}$$


$$I_3'' = \frac{350}{55} \Rightarrow I_3'' = 6.36A$$

By using KCL: $I_2'' = I_1'' + I_3''$

$$10 = 3.63 + 6.36$$

$$10 \approx 9.9$$

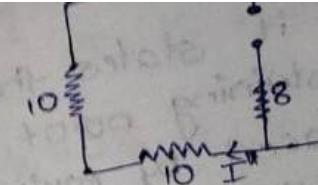Step 4: Let V_2 is acting. V is short circuit & $10A$ is open.



Total resistance of

$$R_T = 10 + 10 + 10 + 10 = 40\Omega$$

$$R_T = 55\Omega$$

Total current in

$$I_3''' = \frac{V_2}{R_T}$$

$$I_3''' = 0$$

Current flowing

$$I_1''' =$$

current flowing

$$I_2''' =$$

By using

Incident set

step 5:

The re

The resultant



$$I_r = 0$$

$$I_1 =$$

The result

The resu

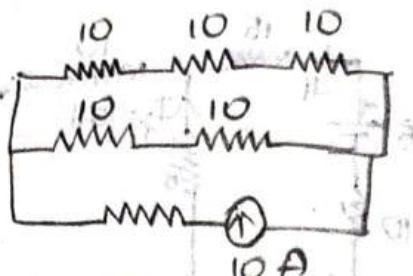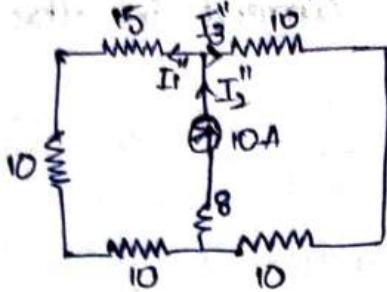Step 3: Let $10A$ is acting & V_2 is short circuit



Total resistance of the circuit R_{T2} is

$$R_{T2} = 10 + 10 = 20 \text{ (series)}$$

$$10 + 10 + 15 = 35 \text{ (series)}$$

$$(R_{T2} = \frac{20 \times 35}{20 + 35} \Rightarrow R_{T2} = \frac{700}{55})$$

$$R_{T2} = 12.72 \Omega \text{ (parallel)}$$

$$R_{T2} = 12.72 + 8$$

$$= 20.72 \text{ (series)}$$

$$\therefore R_{T2} = 20.72 \Omega$$

\therefore Total current flowing through the circuit

$$I_2'' = 10A \text{ (given)}$$

Current flowing through 15Ω

$$I_1'' = I_2'' \times \frac{20}{20+35} \Rightarrow I_1'' = 10 \times \frac{20}{55}$$

$$I_1'' = \frac{400}{55} \Rightarrow I_1'' = 7.27 A$$

current flowing through 10Ω

$$I_3'' = I_2'' \times \frac{35}{35+20} \Rightarrow I_3'' = 10 \times \frac{35}{55}$$


$$I_3'' = \frac{350}{55} \Rightarrow I_3'' = 6.36 A$$

By using KCL:

$$10 = 3.63 + 6.36$$

$$10 \approx 9.9$$

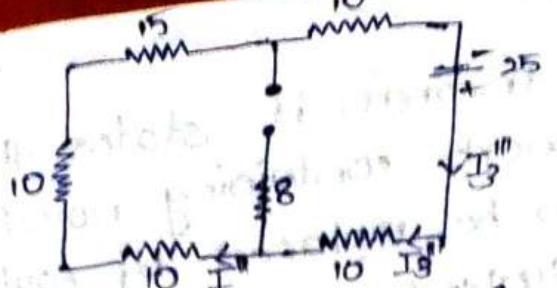Step 4: Let V_2 is acting, V is short circuit & $10A$ is open.



Total resistance of the circuit R_{T3}

$$R_{T3} = 10 + 10 + 10 + 10 + 15 = 55 \Omega$$

$$R_{T3} = 55 \Omega$$

Total current in the circuit

$$I_3''' = \frac{V_2}{R_{T3}} \Rightarrow I_3''' = \frac{25}{55}$$

$$I_3''' = 0.45 A$$

Current flowing through 10Ω

$$I_1''' = I_3''' = 0.45 A$$

Current flowing through 8Ω

$$I_2' = 0 A$$

By using KCL: $I_3''' = I_1''' + I_2'$

$$0.45 = 0.45 + 0$$

$$0.45 = 0.45$$

Step 5: The resultant direction of current in the circuit

The resultant direction of current $I_1 = I_1''' - I_1'' + I_1'''$

$$I_1 = 0.27 - 6 - 3.63 + 0.45$$

$$I_1 = -2.91 A$$

The resultant direction of current $I_2 = I_2' + I_2'' + I_2'''$

$$I_2 = 0 + 10 + 0$$

$$I_2 = 10 A$$

The resultant direction of current $I_3 = I_3' + I_3'' + I_3'''$

$$I_3 = 0.27 + 6.36 + 0.45$$


$$I_3 = 7.08 A$$

Thevenins Theorem:


Statement: The Thevenins theorem states that any two terminals linear network containing no. of voltage source and resistance can be replaced by equivalent circuit consisting of equivalent voltage (V_{TH}) is connected with series equivalent resistance [R_{TH} element].

Explanation/Verification of Thevenins Theorem:

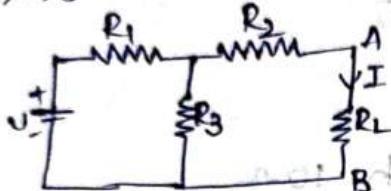
- Determine the current through R load (R_L) by using thevenins theorem in the circuit shown in fig.



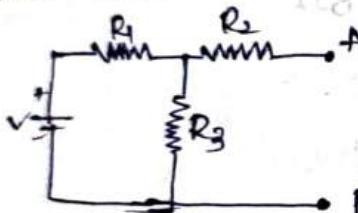
- Step 1: Remove the load resistance (R_L) b/w the terminal A and B in the circuit shown in fig.



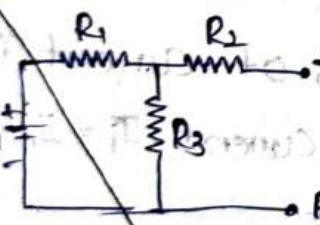- Step 2: Remove the load resistance (R_L) b/w the terminal 1 A and B in the circuit shown in fig.



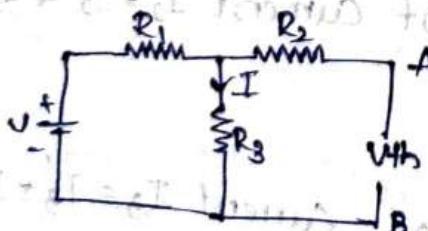- Step 2: calculate the thevenins voltage (V_{TH}) b/w the terminal A and B in the circuit shown in fig.



The open circuit b/w the terminal A and B the internal resistance of R_2 value will be "zero"


The internal resistance $[R_T = R_1 + R_2]$

According to ohm's law where $I = \frac{V}{R}$

$$I = \frac{V}{R_T} \Rightarrow V_I = \frac{V}{(R_1 + R_2)}$$


$$V_{Th} > IR_3 \Rightarrow V_{Th} = \frac{V}{(R_1 + R_2)} \times R_3$$

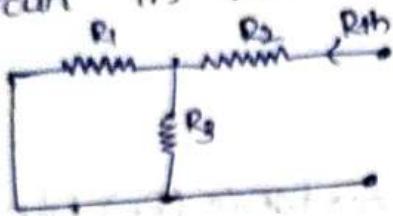Step-3: calculate the equivalent resistance can be replaced by voltage source are short circuit either current source or open circuit in the circuit shown in fig.




$$R_{Th} = \frac{R_1 \times R_3}{R_1 + R_3} + R_2$$

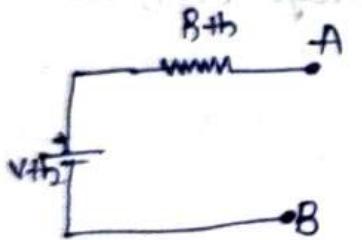Step-4: Draw the equivalent circuit can be replaced by thevenins voltage (V_{Th} element) we should connect in series with Thevenins resistance (R_{Th}) in the circuit shown in fig.



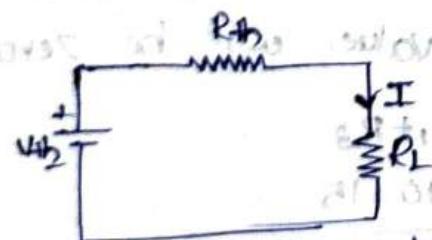Step-5: Reconnect the load resistance b/w the terminal A and B where it is removed in the circuit shown in fig.




Step-6: Determine the current through R_L above circuit shown in fig. According to ohm's law

$$I = \frac{V}{R} \Rightarrow I = \frac{V_{Th}}{R_{Th} + R_L} \quad (\because R = R_{Th} + R_L)$$


$$I_{Ths} = I$$

$$0.1 \times 38.0 = 4V < 4.9I = 4V$$

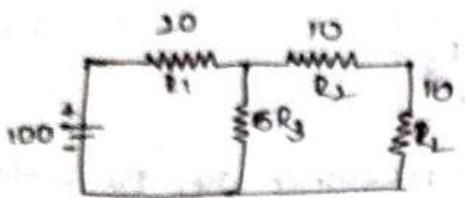
Q) Determine the current through RL resistor by using Thevenin's Theorem in the circuit shown in fig.




Sol:

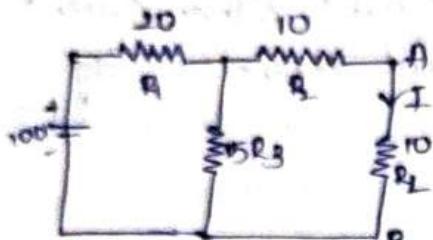

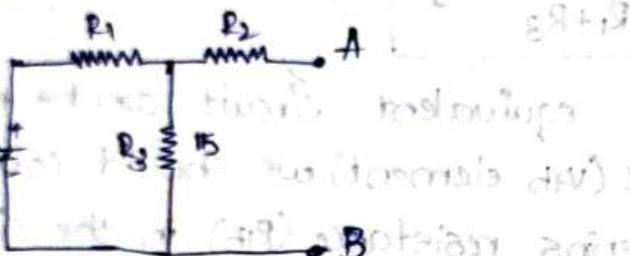Step 1: Remove the load resistance (R_L) b/w the terminal A & B in the circuit.



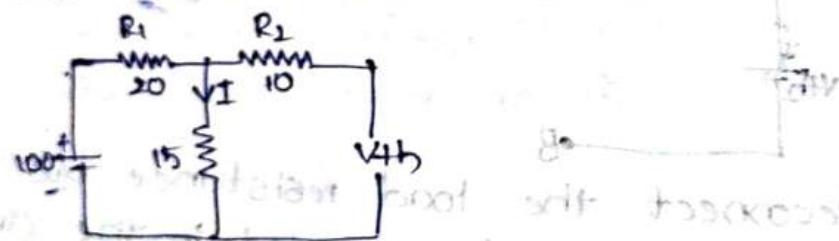Step 2: calculate the thevenin's voltage (V_{th}) b/w the terminal A & B in the circuit.



The open circuit b/w the terminal A & B the internal resistance of R_2 value will be zero.

The total resistance $R_T = R_1 + R_3$

$$R_T = 20 + 15$$

$$R_T = 35$$

According to Ohm's law where $I = \frac{V}{R}$


$$I = \frac{V}{R_T} \Rightarrow I = \frac{100}{35}$$

$$I = 2.85A$$

$$V_{th} = IR_3 \Rightarrow V_{th} = 2.85 \times 15$$

$$V_{th} = 42.75V$$

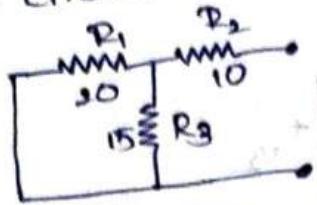Step 3: calculate the equivalent resistance can be replaced by voltage source are short-circuit. Either current source are open circuit in the circuit shown in fig.





$$R_{th} = \frac{20 \times 15}{20 + 15} \rightarrow \frac{300}{35} = 8.57 \Omega$$


$$R_{th} = 8.57 + 10$$

$$\boxed{R_{th} = 18.57}$$

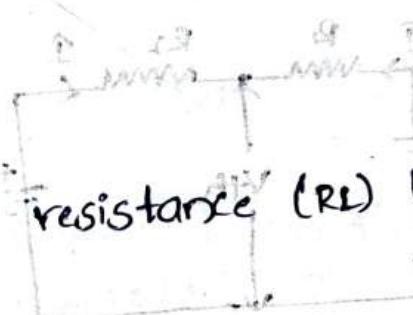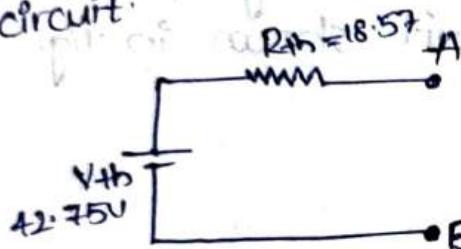Step 4: Draw the equivalent circuit can be replaced by the thevenins voltage (V_{th}) elements) we should connect in series with thevenins resistance (R_{th}) in the circuit.



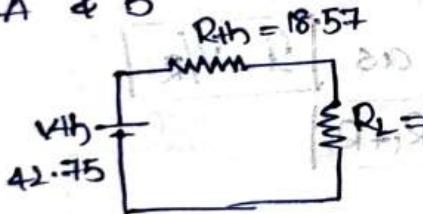Step 5: Reconnect the load resistance (R_L) b/w the terminals A & B



$$I = \frac{V}{R}$$

$$R = 18.57 + 10$$

$$R = 28.57$$

$$I = \frac{42.75}{28.57}$$


$$I = \frac{42.75}{28.57}$$

$$\boxed{I = 1.49A}$$


$$\frac{V - V}{R_{th}} \leftarrow \frac{V}{R_{th}} = I$$

$$\frac{V - V}{R_{th}}$$

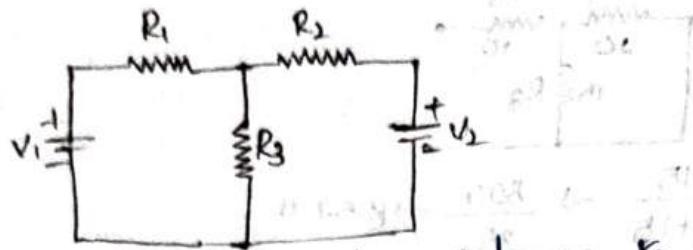
→ Determine the current through R_3 resistance by using Termination's theorem in the circuit shown in fig.



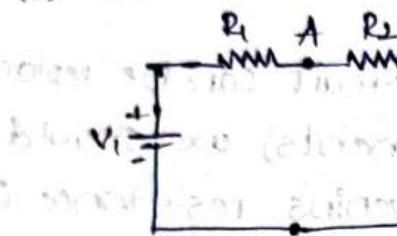Step 1: Remove the load resistance R_3 b/w the terminal A & B in the circuit shown in fig.



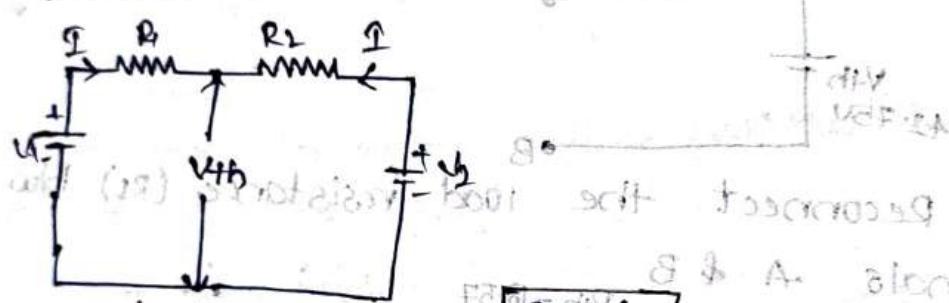Step 2: calculate the equivalent voltage (with the help of the terminal in the circuit shown in fig.)



The total current is given as $I = V/R$.

The total resistance

$$R_T = R_1 + R_2$$

$$I = V/R_T \Rightarrow \frac{V_1 - V_2}{R_1 + R_2}$$

$$\frac{V_2 - V_1}{R_1 + R_2}$$

The voltage terminal passing through +ve and the voltage drop is decreased

$$V_{th} = V_1 - IR_1 \quad \text{--- (1)}$$

$$V_{th} = V_1 - \frac{(V_1 - V_2)}{R_1 + R_2} \times R_1$$

$$V_{th} = \frac{V_1 R_1 + V_1 R_2 - V_1 R_1 + V_2 R_1}{R_1 + R_2}$$

$$V_{th} = \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}$$

The voltage passing through -ve and the voltage drop will increases.


$$V_{th} = V_2 - IR_2 \quad \text{--- ②}$$

$$V_{th} = V_2 - \left(\frac{V_2 - V_1}{R_1 + R_2} \right) \times R_2$$

$$V_{th} = \frac{V_2 R_1 + V_2 R_2 - V_1 R_2 + V_1 R_2}{R_1 + R_2}$$


$$V_{th} = \frac{V_2 R_1 + V_1 R_2}{R_1 + R_2}$$

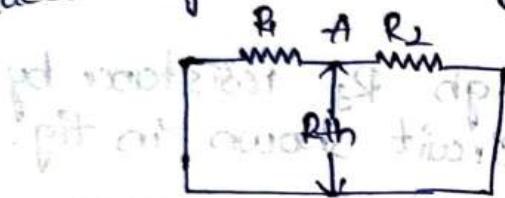Step.3: Determine the equivalent resistance (R_{th}) can be replaced by the voltage sources (V_1, V_2 : short circuit)




$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2}$$

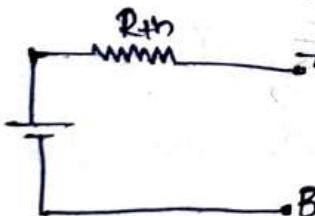Step.4: Draw the equivalent circuit consisting of equivalent voltage (V_{th}) is connected with series, equivalent resistance (R_{th}).



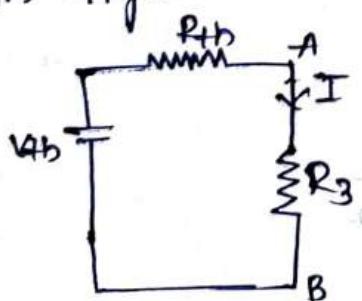Step.5: Reconnect the load resistance b/w the terminal A & B and determine the current in the circuit shown in figure.



$$I = \frac{V_{th}}{R_{th} + R_3}$$

$$I = \frac{V}{R_T}$$

According to ohm's law


Sub R₁ & R₂ in

$$I = \frac{\frac{V_1 + V_2 R_1}{R_1 + R_2}}{\frac{R_1 \times R_2}{R_1 + R_2} + R_3}$$

$$I = \frac{\frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}}{R_1 R_2 + R_1 R_3 + R_2 R_3 + R_1 + R_2}$$

$$I = \frac{V_1 R_2 + V_2 R_1}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

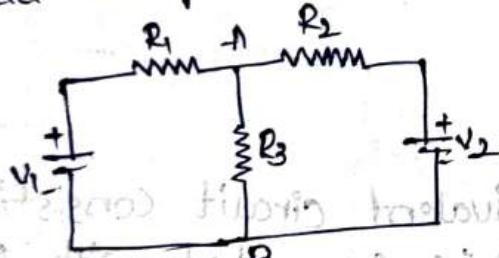→ Determine the current through R₃ resistance by using nodal analysis in the circuit shown in fig.



$$\frac{Sx, S}{S+1, S} = dS$$

by using nodal analysis

$$0 = \frac{V_{4b} - V_1}{R_1} + \frac{V_{4b}}{R_3} + \frac{V_{4b} - V_2}{R_2}$$

$$V_{4b} = IR_3$$

$$0 = \frac{IR_3 - V_1}{R_1} + \frac{IR_3}{R_3} + \frac{IR_3 - V_2}{R_2}$$

$$0 = \frac{IR_3}{R_1} - \frac{V_1}{R_1} + I + \frac{IR_3 - V_2}{R_2}$$

$$\frac{IR_3}{R_1} + I + \frac{IR_3}{R_2} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$I \left(\frac{R_3}{R_1} + 1 + \frac{R_3}{R_2} \right) = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$\text{I} \left(\frac{R_2 R_3 + R_1 R_2 + R_1 R_3}{R_1 R_2} \right) = \frac{V_1 R_2 + V_2 R_1}{R_1 R_2}$$

$$\text{I} (R_2 R_3 + R_1 R_2 + R_1 R_3) = V_1 R_2 + V_2 R_1$$

$$\boxed{\text{I} = \frac{V_1 R_2 + V_2 R_1}{R_1 R_2 + R_2 R_3 + R_3 R_1}}$$

$$\text{I} = \frac{100(20) + 70(20)}{(20)(20) + 20(160) + (160)(20)}$$


$$\text{I} = \frac{100 + 70}{20 + 160 + 160}$$

$$\text{I} = \frac{170}{340}$$


$$= 0.5$$

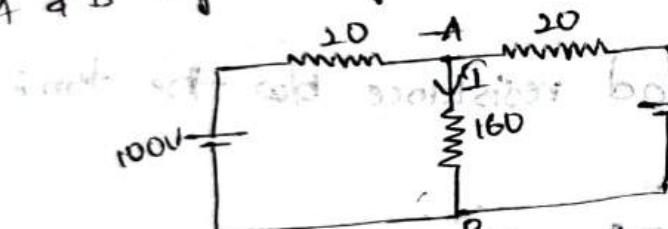Problems:

Determine the current in 160Ω below terminals A & B by using Thvenin's theorem.



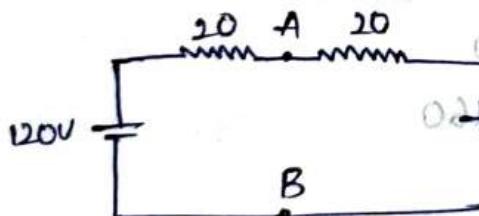Step 1: Remove the load resistance (R_L) below the terminals A & B as shown in fig.



Step 2: calculate the equivalent voltage (V_{TH}) with the terminal in circuit.

$$\text{I} = \frac{V}{R_T} = \frac{V_1 - V_2}{R_1 + R_2}$$

$$\frac{100 - 70}{20 + 20} = \frac{30}{40}$$


$$= 0.75 \text{ A}$$

$$\begin{aligned}V_{th} &= V_1 - I R_1 \\&= 100 - (0.75) (20) \\&= 100 - 15\end{aligned}$$

$$[V_{th} = 85 \text{ V}]$$

The voltage terminals passing through +ve and the voltage drop will be decreased]

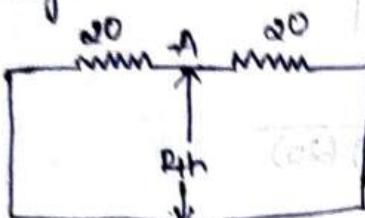
Step 3: Determine the equivalent resistance can be replaced by the voltage sources (V_1, V_2)




$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{20 \times 20}{20 + 20} = \frac{400}{40}$$

$$[R_{th} = 10 \Omega]$$

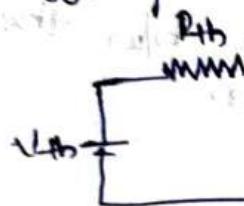Step 4: Draw the equivalent circuit consisting of equivalent voltage (V_{th}) is connected in series



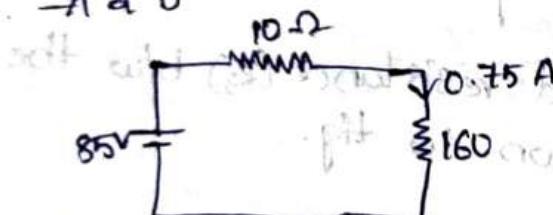Step 5: Reconnect the load resistance between the terminal A and B.



According to Ohm's law

$$I = \frac{V_{th}}{R_T}$$

$$R_T = 10 + 160 \\= 170$$

$$I = \frac{85}{170}$$


$$[I = 0.5 \text{ A}]$$

$$\frac{V_A}{V_B} = \frac{I}{I+I_L}$$

$$\frac{0.5}{0.5} = \frac{0.5 + 0.75}{0.5 + 0.75}$$

$$A = 0.5$$

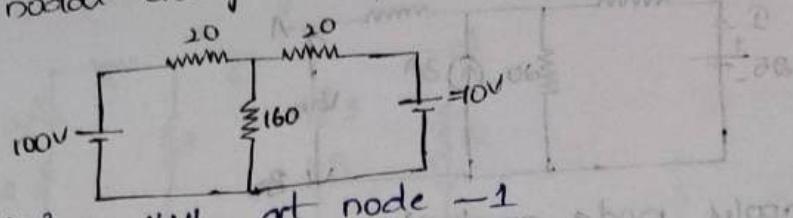→ Determine the current through R_3 resistance by using nodal analysis.



By applying KVL at node -1

$$0 = \frac{V_{th} - 100}{20} + \frac{V_{th}}{160} + \frac{V_{th} - 10}{20}$$

$$0 = \frac{8V_{th} - 800 + 14V_{th} + 8V_{th} - 560}{160}$$


$$0 = \frac{17V_{th} - 1360}{160}$$

$$17V_{th} - 1360 = 0$$

$$V_{th} = \frac{1360}{17}$$

$$\boxed{V_{th} = 80 \text{ V}}$$

R_{th}

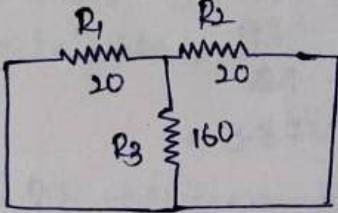

$$R_{th} = \frac{R_1 \times R_3}{R_1 + R_3} + R_2$$

$$R_{th} = \frac{20 \times 160}{20 + 160} + 20 \quad \text{not Rth if}$$

$$= \frac{3200}{180} + 20$$


$$= 17.7 + 20$$

$$\boxed{R_{th} = 37.7 \Omega}$$

$$V_{th} = IR$$

$$I = \frac{V_{th}}{R_3} = \frac{80}{160}$$

$$= 0.5$$

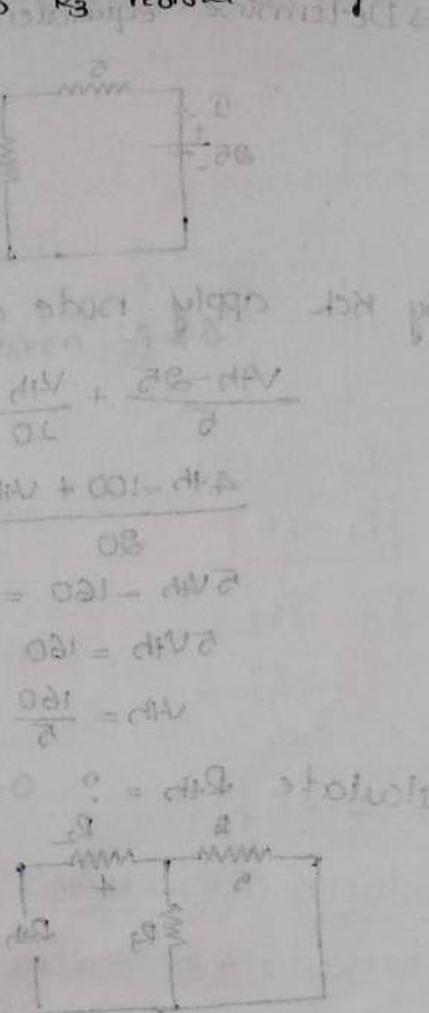


$$0 = \frac{10 \times 20}{20 + 160} = 0.5$$


$$0 = \frac{0.5 \times 20}{20 + 160} = 0.5$$

$$0 = \frac{0.5 \times 160}{20 + 160} = 0.5$$

$$\boxed{0.5 = 0.5}$$

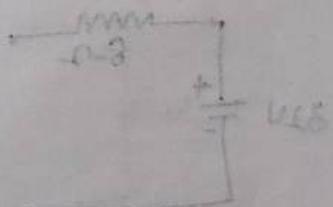

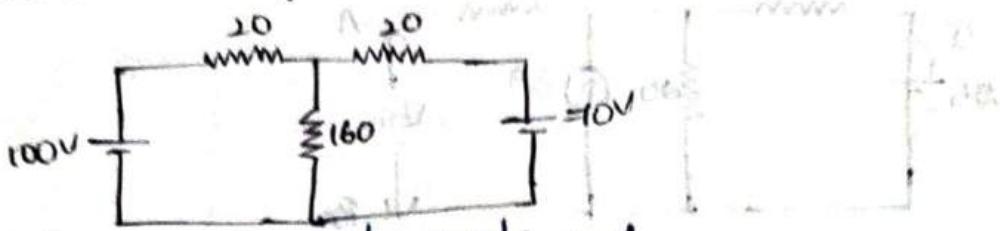⇒ Determine the current through R_3 resistance by using nodal analysis.



By applying KVL at node -1

$$0 = \frac{V_{th} - 100}{20} + \frac{V_{th}}{160} + \frac{V_{th} - 10}{20}$$

$$0 = \frac{8V_{th} - 800 + 14V_{th} + 8V_{th} - 560}{160}$$


$$0 = \frac{17V_{th} - 1360}{160}$$

$$17V_{th} - 1360 = 0$$

$$V_{th} = \frac{1360}{17}$$

$$\boxed{V_{th} = 80 \text{ V}}$$

R_{th}

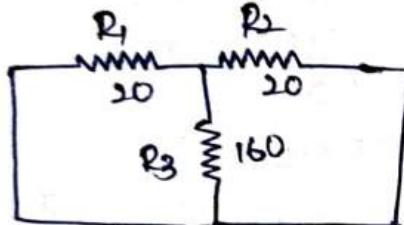

$$R_{th} = \frac{R_1 \times R_3}{R_1 + R_3} + R_2$$

$$R_{th} = \frac{20 \times 160}{20 + 160} + 20 \Leftrightarrow R_{th} \neq$$

$$= \frac{3200}{180} + 20$$

$$= 17.7 + 20$$

$$\boxed{R_{th} = 37.7 \Omega}$$

$$V_{th} = IR$$

$$I = \frac{V_{th}}{R_3} = \frac{80}{160}$$

$$= 0.5$$



$$0 = 0.21 - 0.21 \alpha$$

$$0.21 = 0.21 \alpha$$

$$\alpha = \frac{0.21}{0.21} = 1$$



$$0 + \frac{0.21 \times 1.9}{0.21 + 1.9} = 0.21$$

$$0 + \frac{0.21 \times 0}{0.21 + 0} = 0$$

$$0 + \frac{0.01}{0.21} = 0$$

$$\boxed{0.21 - 0.21 \alpha}$$

∴ $\alpha = 0.21$



$\therefore R_{th} = 0.21 \times 160 = 33.6 \Omega$